
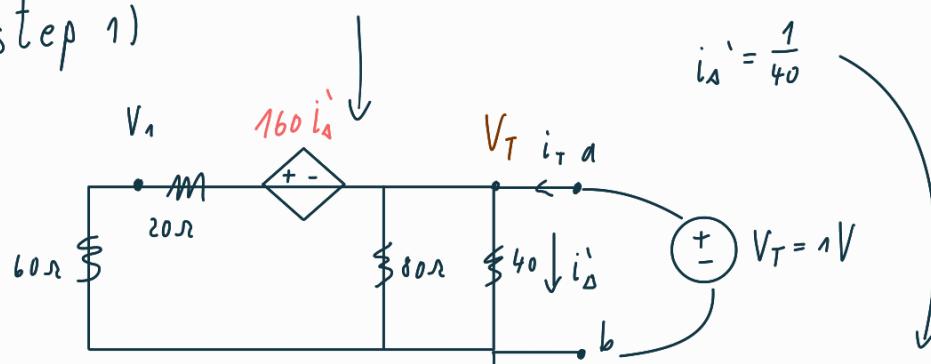


step 1)

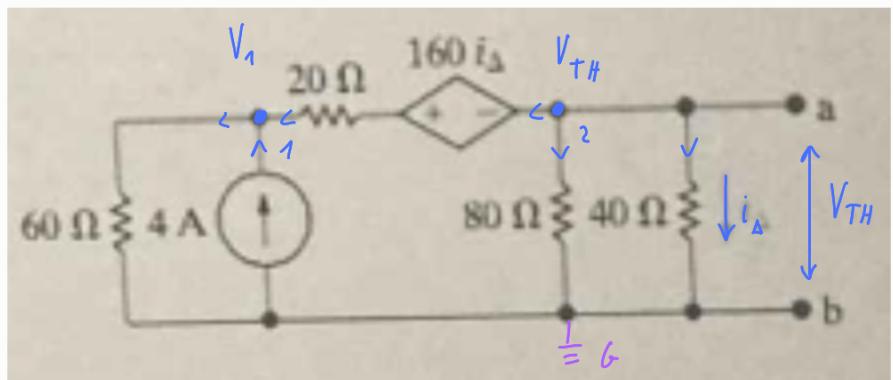


$$i_T - \frac{1}{40} - \frac{1}{80} - \left(\frac{V_T - (-160i_\Delta)}{60 + 20} \right) = i_T - \frac{3}{80} - \left(\frac{1 + \frac{160}{40}}{80} \right) \Rightarrow i_T = \frac{3}{80} + \frac{1 + 4}{80} = \frac{1}{10}$$

$$R_{TH} = \frac{V_T}{i_T} = \frac{1}{\frac{1}{10}} = 10 \Omega$$




$$\text{Node 1: } \frac{V_{TH} + 160i_\Delta - V_1}{20} + 4 - \frac{V_1}{60} = 0 \Rightarrow V_{TH} = 30$$
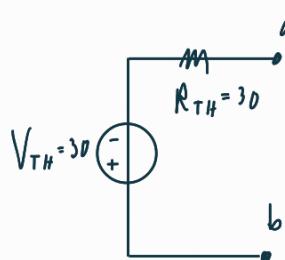
$$\text{Node 2: } \frac{V_{TH}}{40} + \frac{V_{TH}}{80} + \frac{V_{TH} + 160i_\Delta - V_1}{20} = 0$$




, for max. power: 30

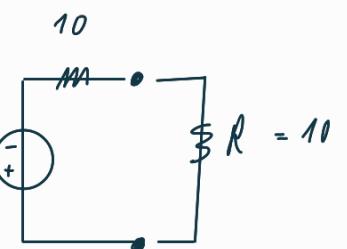

$$P = \frac{V_{TH}^2}{4R_{TH}} = \frac{900}{40} = \frac{90}{4} = \frac{45}{2} = 22.5 W$$

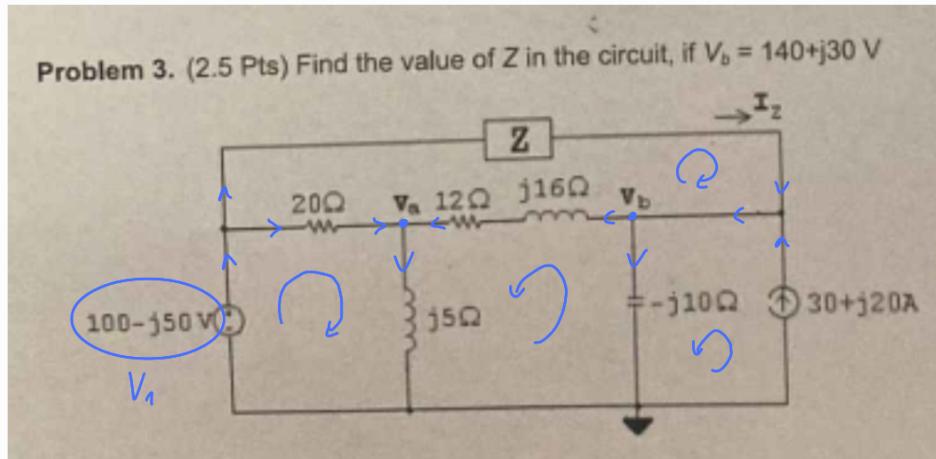Problem 3. (2.5 Pts) Find the value of Z in the circuit, if $V_b = 140+j30 \text{ V}$




$$\text{node } a: \frac{V_1 - V_a}{20} + \frac{V_b - V_a}{12 + 16j} - \frac{V_a}{5j} = 0 \Rightarrow Z = 2 + 2j$$


$$\text{node } b: 30 + 20j + \frac{V_1 - V_b}{Z} - \frac{V_b}{-10j} - \frac{V_b - V_a}{12 + 16j} = 0$$

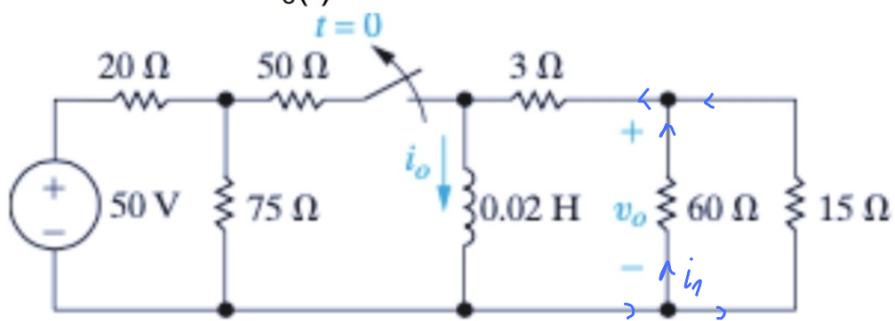1. The switch has been closed for a long time. At $t = 0$ the switch is opened.

 - Determine $i_o(0)$ for $t \geq 0$.
 - Determine $v_o(t)$ for $t \geq 0+$.




for $t < 0$:

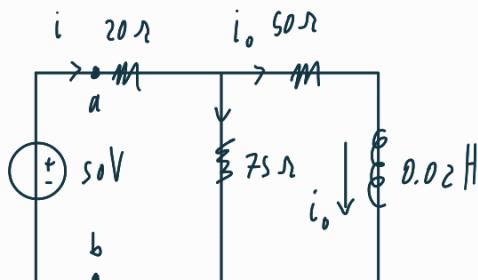

$$R_{eq} = \frac{50 \cdot 75}{50 + 75} + 20 = 30 + 20 = 50 \Rightarrow i = \frac{U}{R} = \frac{50}{50} = 1$$

$$i_o = i \cdot \frac{75}{125} = 1 \cdot \frac{3}{5} = \frac{3}{5}$$

for $t \geq 0$:

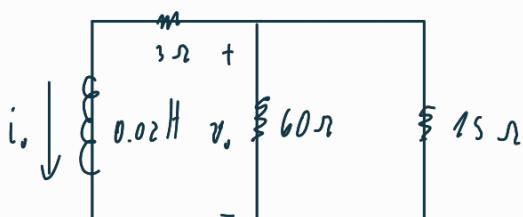

$$\tau = \frac{L}{R_{eq}} = \frac{0.02}{15} = \frac{2}{1500} = \frac{1}{750}$$


$$R_{eq}^1 = 3 + \frac{4 \cdot 15 \cdot 15}{5 \cdot 15} = 3 + 12 = 15 \Omega$$

$$i(t) = i_o \cdot e^{-\frac{t}{\tau}} = \frac{3}{5} \cdot e^{-750t}$$

$$i_1(t) = i(t) \cdot \frac{1}{2s} = \frac{3}{s} \cdot e^{-750t} \cdot \frac{1}{s} = \frac{3}{2s} \cdot e^{-750t}$$

$$v_o(t) = L \cdot \frac{di_1(t)}{dt} = 0.02 \cdot \left(\frac{3}{2s} \cdot e^{-750t} \right)' = \frac{2}{100} \cdot \frac{3}{2s} \cdot (-750) \cdot e^{-750t} = \frac{-3 \cdot 750}{1250} e^{-750t} = -\frac{9}{s} e^{-750t}$$

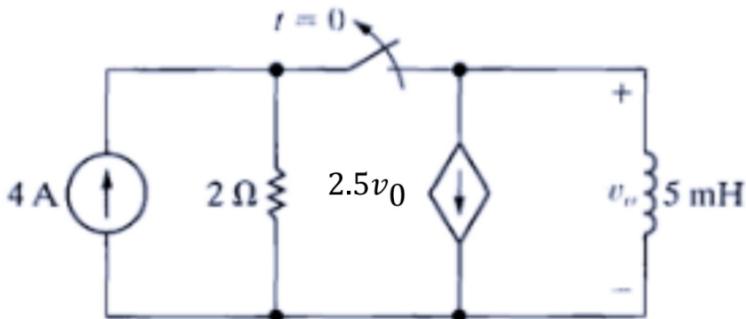
2. The switch in the circuit below has been closed for a long time before opening at $t = 0$. Find $v_o(t)$ for $t \geq 0^+$.



$$\text{for } t < 0 \quad i_s = 4A$$



for $t \geq 0^+$:

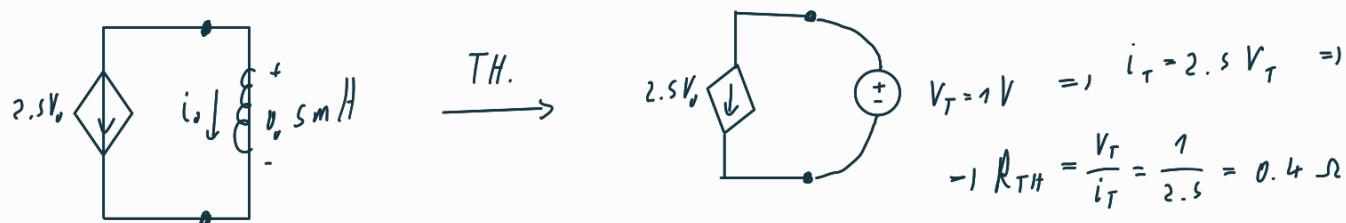


$$\tau = \frac{L}{R} = \frac{s \cdot 10^{-3}}{4 \cdot 10^{-4}} = \frac{s}{4} \cdot 10^{-2} = \frac{125}{100} \cdot 10^{-2} = 1.25 \cdot 10^{-2} = 0.0125$$


$$i(t) = i_s e^{-\frac{t}{\tau}} = 4 \cdot e^{-\frac{10000t}{125}} = 4 \cdot e^{-80t}$$

$$v_o(t) = L \frac{di(t)}{dt} = 5 \cdot 10^{-3} \cdot 4 \cdot (-80) \cdot e^{-80t} = -1.6 \cdot e^{-80t}$$

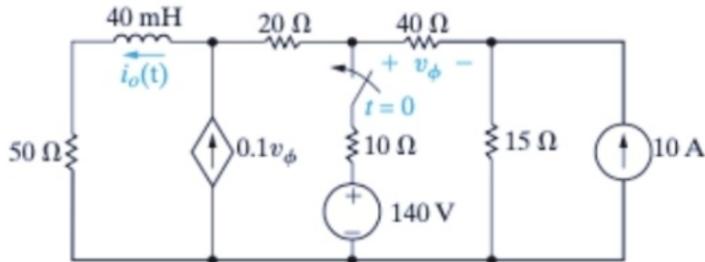3. The switch in the circuit has been opened a long time before closing at $t = 0$. Find $i_o(t)$ for $t \geq 0$



for $t < 0$:

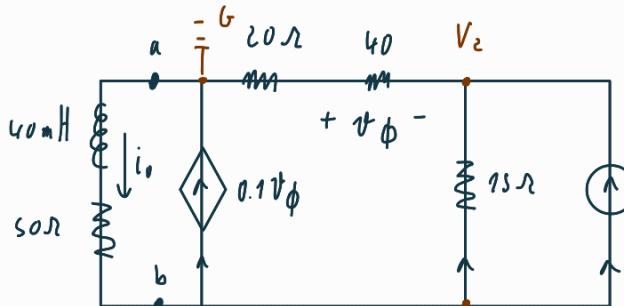



$$1: \frac{-V_1}{50} - 0.1v_\phi - \frac{V_1 - V_2}{15} - 10 = 0$$

$$2: 10 + \frac{V_1 - V_2}{15} - \frac{V_2}{60} = 0$$

$$v_\phi = -V_2 \cdot \frac{40}{60}$$

$$\Rightarrow V_1 = -300 \text{ V} \Rightarrow i_o \cdot \frac{-(-300)}{50} = 6 \text{ A}$$

for $t \geq 0^+$

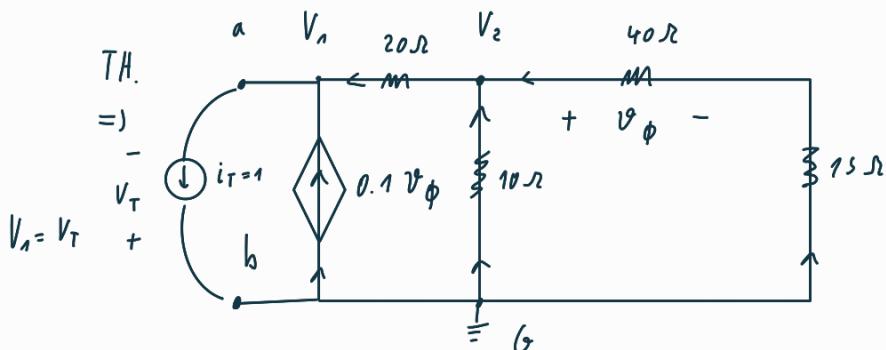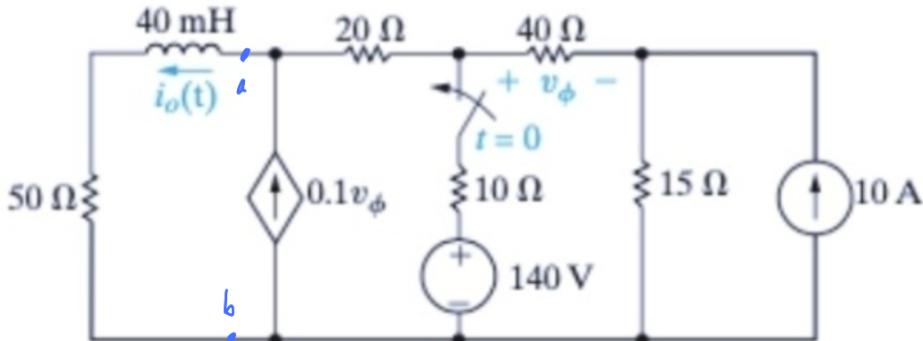

$$0.1v_\phi + \frac{V_2 - V_1}{20} - 1 = 0$$


$$V_1 = -74$$

$$-\frac{V_2}{10} - \frac{V_2}{55} - \frac{V_2 - V_1}{20} = 0$$


$$V_T = -V_1 = 74$$

$$v_\phi = -\left(-V_2 \cdot \frac{40}{55}\right)$$

$$R_{Th} = \frac{V_T}{i_r} = 74 \Omega$$

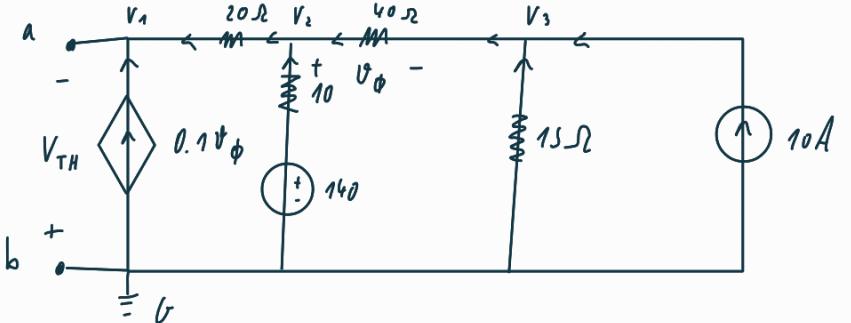

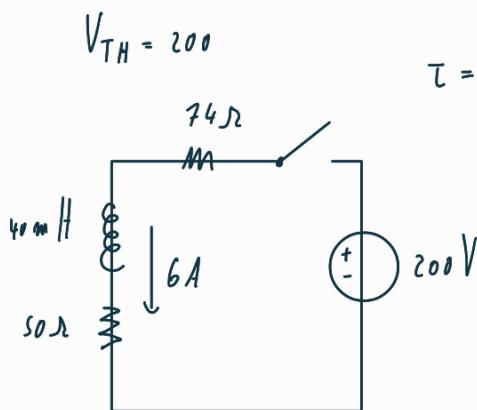
$$\begin{aligned}\frac{V_3 - V_2}{10} + \frac{V_2 - V_1}{20} &= 0 \\ \frac{V_2 - V_1}{20} &= \frac{V_3 - V_2}{40} + \frac{V_2 - 140}{10} \\ -\frac{V_3}{15} + 10 &= \frac{V_3 - V_2}{40}\end{aligned}$$




5. The switch in the circuit has been in position **a** for a long time. At $t = 0$, the switch moves instantaneously to position **b**. For $t \geq 0^+$, find

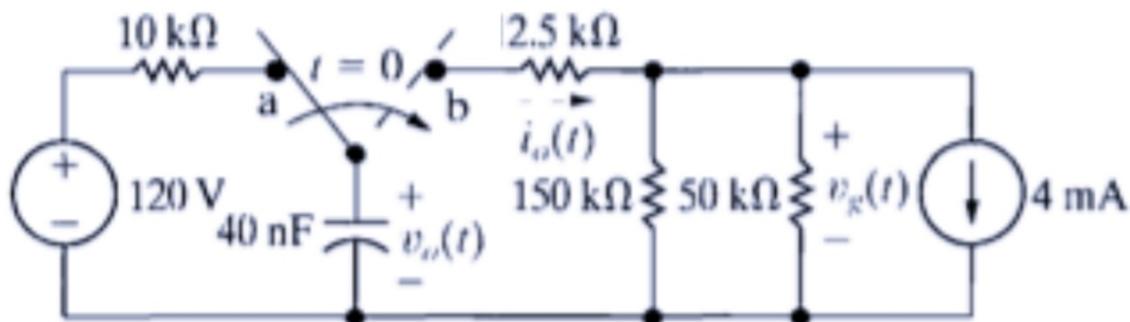- a. $v_o(t)$
- b. $i_o(t)$
- c. $v_g(t)$
- d. $v_g(0^+)$



for $t \leq 0$: $10k\Omega$

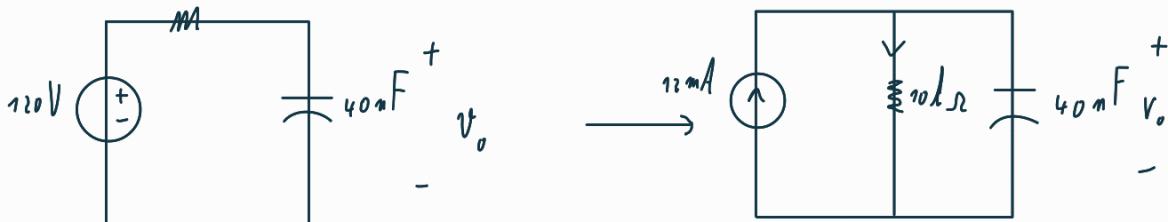


for $t \geq 0^+$:


$$V_o = 1 \cdot R = 120 \text{ V}$$

$$R_{eq} = 2.5 + \frac{3 \cdot 50 \cdot 50}{4 \cdot 50} = 2.5 + 37.5 = 40 \text{ k}\Omega$$


$$\tau = RL = 40 \cdot 1000 \cdot 40 \cdot 10^{-3} = 1600 \cdot 10^{-6} = 1.6 \cdot 10^{-3} = \frac{8}{5000}$$

$$R_1 = 37.5$$

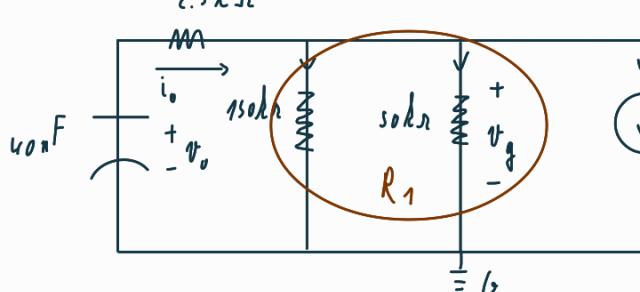

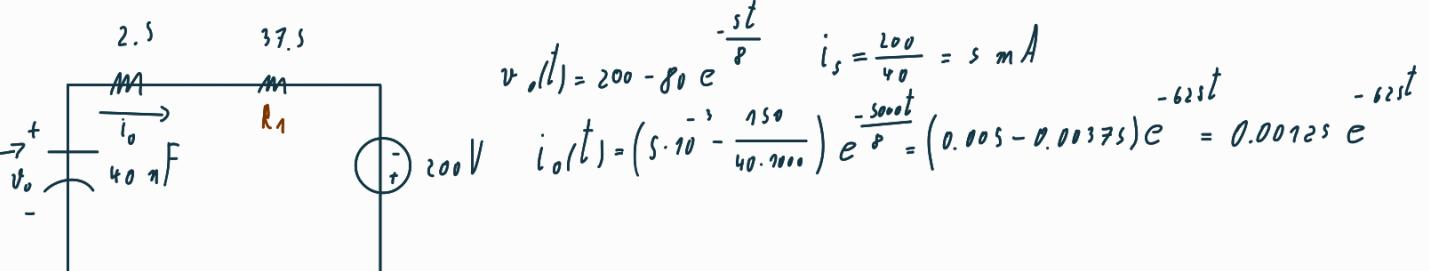

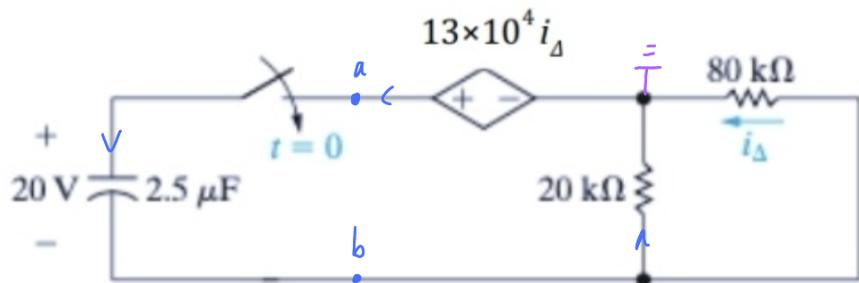6. a. The capacitor in the circuit below is charged to 20 V at the time the switch is closed. If the capacitor ruptures when its terminal voltage equals or exceeds 20 kV, how long does it take to rupture the capacitor?



Given values: $V_s = 20 V$, $C = 2.5 \mu F$, $R_1 = 20 k\Omega$, $R_2 = 80 k\Omega$, $i_A = 13 \times 10^4 i_A$

Equations:

$$V_A = 130 \cdot 10^3 i_A + V_T = 130 \cdot 10^3 \frac{V_A}{80 \cdot 10^3} + V_T = 1 \quad V_A = \frac{V_T}{1 - \frac{13}{8}} = \frac{V_T}{-\frac{5}{8}}$$

$$i_A = \frac{V_A}{80 \cdot 10^3},$$


$$i_T = \frac{V_A}{20 \cdot 10^3} - \frac{V_A}{80 \cdot 10^3} - V_A \left(\frac{3}{8} \right) = -\frac{8}{5} \cdot \frac{3}{10^3} \cdot V_T = -\frac{3}{5} V_T$$


$$= 1 \quad R_{TH} = \frac{V_T}{i_T} = \frac{V_T}{-\frac{3}{5} V_T} = -\frac{5000}{3} \Omega$$

$$V(t) = 20 \cdot e^{-\frac{t}{\tau}} = 20 \cdot e^{-\frac{-t}{2.5 \cdot 10^{-3} \cdot \frac{5000}{3}}} = 20 \cdot e^{\frac{t}{\frac{125}{100}}} = 20 e^{\frac{125 t}{100}}$$

$$20 e^{\frac{125 t}{100}} = 20000 \quad \Rightarrow \quad e^{\frac{125 t}{100}} = 1000 \quad \Rightarrow \quad \frac{125 t}{100} = \ln 100 \quad \Rightarrow \quad t = \frac{3.5 \ln 10}{125} = \frac{3}{4} \ln 10$$

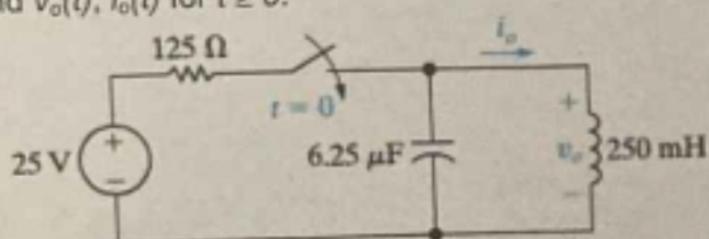Problem 2. (2.5 Pts) There is no energy stored in the circuit below when the switch is closed at $t = 0$. Find $v_o(t)$, $i_o(t)$ for $t \geq 0$.



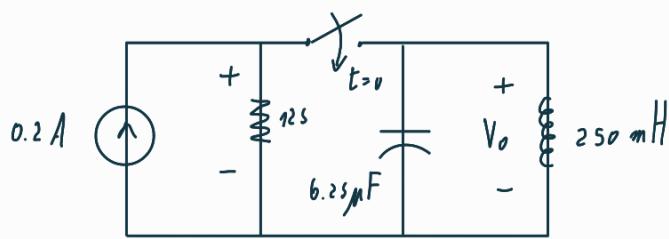

$$V_o(0^+) = ?$$

$\omega_o > \omega$ \Rightarrow underdamp

$$i(t) = i_s + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\zeta t}$$

$$\begin{aligned} \omega_o &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{250 \cdot 10^{-3} \cdot 6.25 \cdot 10^{-6}}} = \frac{1}{\sqrt{25 \cdot 625 \cdot 10^{-10}}} = \\ &= \frac{10^4}{5^3} = 5 \cdot 2^4 = 800 \\ \zeta &= \frac{1}{2RC} = \frac{1}{2 \cdot 128 \cdot 625 \cdot 10^{-8}} = \frac{10^8}{2 \cdot 5^7} = 5 \cdot 2^7 = 640 \\ \omega_d &= \sqrt{\omega_o^2 - \zeta^2} = 480 \end{aligned}$$

$$i_s(t) = 0.2 - (0.2 \cos 480t + 0.26 \sin 480t) e^{-640t}$$

$$v_o(t) = L \frac{di}{dt} = 250 \cdot 10^{-3} \cdot \left((128 \sin 480t - 128 \cos 480t) e^{-640t} - 640 (-0.2 \cos 480t - \frac{4}{15} \sin 480t) e^{-640t} \right)$$

$$\left(i_s + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\zeta t} \right)' = \left(-\omega_d B_1 \sin \omega_d t + \omega_d B_2 \cos \omega_d t + (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\zeta t} \right) e^{-\zeta t}$$

