


$$\sum_{i=1}^n p_i = 0 \quad n - \text{nr. of elements in the circuit}$$

$$\sum_{j=1}^n i_j = 0 \quad n - \text{nr. of branches that are connected to the node} = KCL$$

$$\sum_{i=1}^n V_i = 0 \quad n - \text{nr. of element in the loop} = KVL$$

$$I = \frac{V}{R}$$
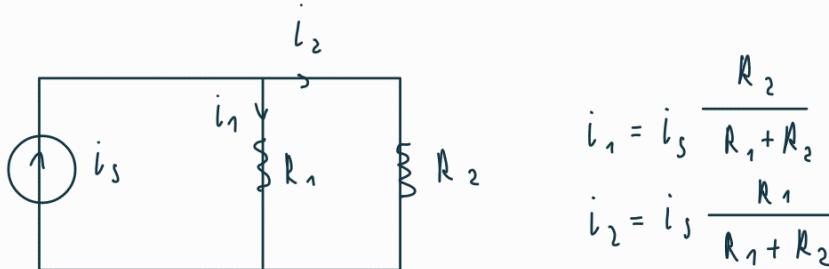
$$P = V \cdot I = I^2 \cdot R = \frac{V^2}{R} \quad ; \text{ in AC} \quad P = \frac{1}{2} I^2 Z$$




$$\begin{cases} R_1 = \frac{R_b R_c}{R_a + R_b + R_c}, \\ R_2 = \frac{R_c R_a}{R_a + R_b + R_c}, \\ R_3 = \frac{R_a R_b}{R_a + R_b + R_c}. \end{cases}$$

(Δ-to-Y)

$$\begin{cases} R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}, \\ R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}, \\ R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}. \end{cases}$$

(Y-to-Δ)

NVM, MCM

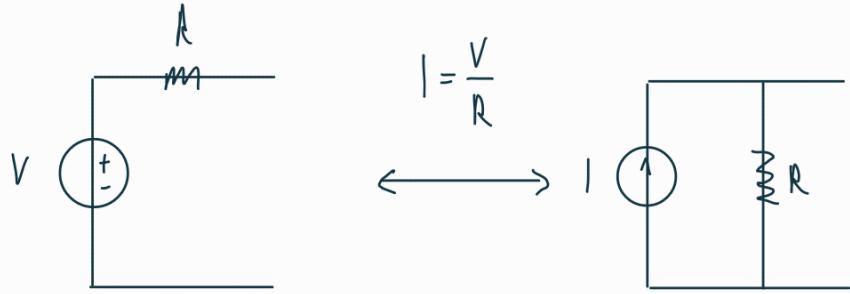

Method 2 to only get R_{Th} alone

For circuits with or without dependent sources:

Step 1: Deactivate all independent sources;

Step 2: Apply a test voltage v_T or test current i_T source to the designated terminals;

Step 3: Calculate the terminal current i_T if a test voltage v_T source is used and vice versa;

Step 4: Get the Thévenin resistance by $R_{Th} = \frac{v_T}{i_T}$

$$m_2 \times P = R_o = R_{TH}$$

superposition

$$W = \frac{1}{2} I^2 L \quad Z_L = j\omega L$$

$$W = \frac{1}{2} V^2 C \quad Z_C = \frac{1}{j\omega C}$$

inductors \Rightarrow resistors

capacitor \Rightarrow resistors $^{-1}$

$$\lambda = \frac{M}{\sqrt{L_1 L_2}}$$

$$I = \frac{V}{Z}$$

g. 13 for Thevenin in AC circuits

$Z_{Th} = (100 + j1600) + Z_r$, where Z_r is the reflected impedance of Z_{11} due to the transformer:

$$Z_{11} = (500 + j100) + (200 + j3600) = (700 + j3700) \Omega$$

$$Z_r = \left(\frac{\omega M}{|Z_{11}|} \right)^2 Z_{11}^* = \left(\frac{1200}{|700 + j3700|} \right)^2 (700 - j3700)$$

$$Z_{Th} = (100 + j1600) + Z_r = (171.09 + j1224.26) \Omega$$

! $j = i$ from complex numbers $j^2 = -1$ etc.

for $+$ / $-$



for $\cdot / :$



rectangular
form

polar form

$$a + b j = A e^{j\theta} = A(\cos \theta + j \sin \theta) = A < \theta = A \cos(wt + \theta)$$

$$A = \sqrt{a^2 + b^2} \quad \theta = \arctan \frac{b}{a}$$


$$\frac{1}{j} = \frac{j}{-1} = -j$$

Assignment 1

1. Given ideal voltage source as shown in figure. Find the wrong answer?

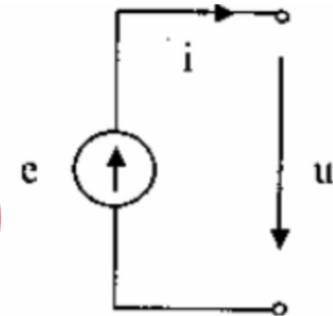
- A. $u \in i$
- B. $u = e$
- C. $u \in e$

*Assignment 4 starts on page 13,
this is recap for me!*




2. Given AC circuit as shown in figure. Which formula is wrong

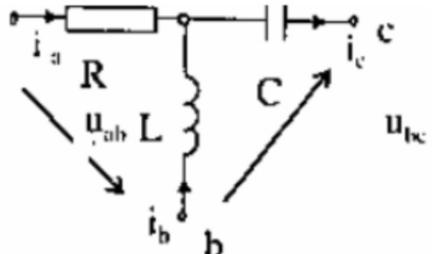- A. $i_a + i_b - i_c = 0$
- B. $i_a + i_b + i_c = 0$
- C. $u_{ab} = R i_a - L \frac{di_b}{dt}$
- D. $u_{bc} = L \frac{di_b}{dt} + 1/C \frac{i_c}{dt}$




3. Given DC source as shown in figure. Find the correct answer?

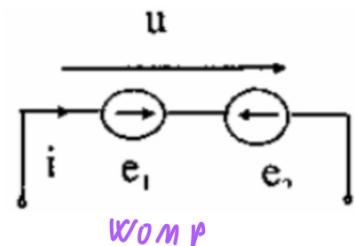- A. $u = e_1 + e_2$
- B. $u = e_2 - e_1$
- C. $u = e_1 - e_2$
- D. $u = e_1 - e_2 - i$




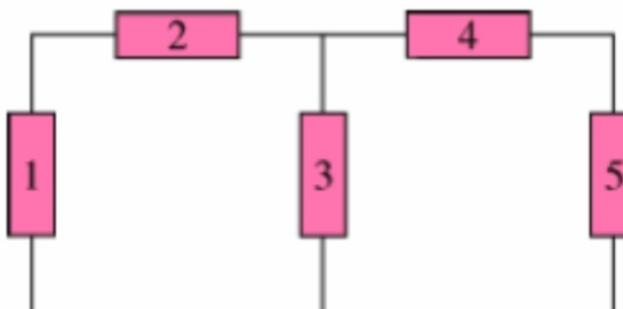4. The figure shows a circuit with five elements. If $p_1 = -200 \text{ W}$, $p_2 = 60 \text{ W}$, $p_4 = 40 \text{ W}$, $p_5 = 30 \text{ W}$. Calculate the power received or delivered by element 3 p_3 .




$$-p_3 = p_1 + p_2 + p_4 + p_5 \Rightarrow -p_3 = -200 + 60 + 40 + 30 \Rightarrow -p_3 = -70 \Rightarrow p_3 = 70$$

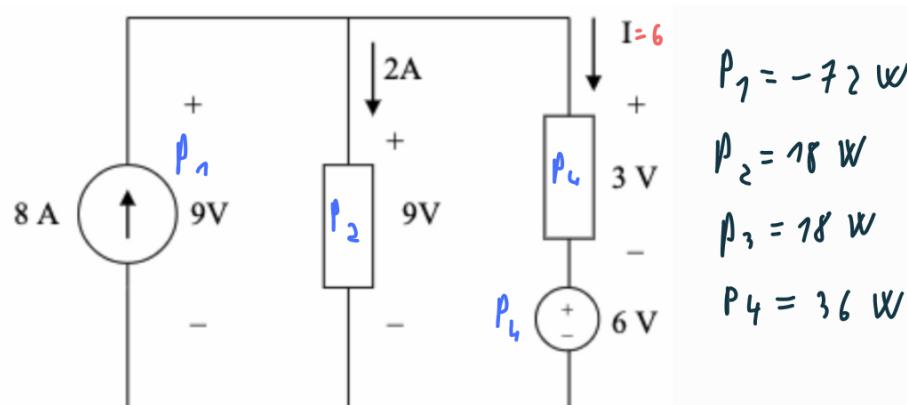5. Find I and P power of each element in the circuit below



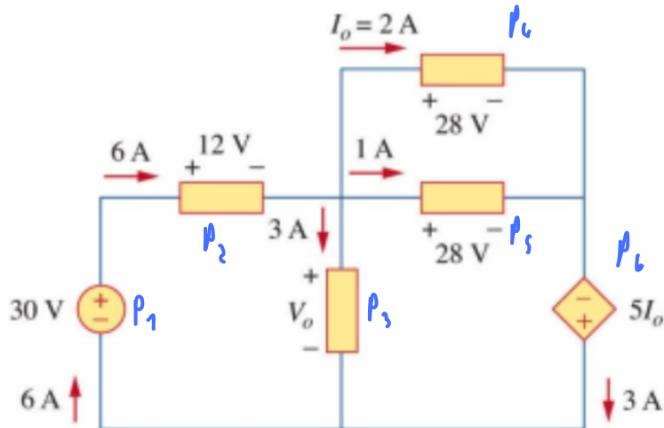6. Find V_o and the power absorbed by each element in the circuit below



$$P_1 = -180 \text{ W}$$

$$P_2 = 72 \text{ W}$$


$$P_4 = 56 \text{ W}$$

$$P_5 = 28 \text{ W}$$

$$P_6 = -10 \text{ W}$$

$$P_3 = 54 \text{ W}$$

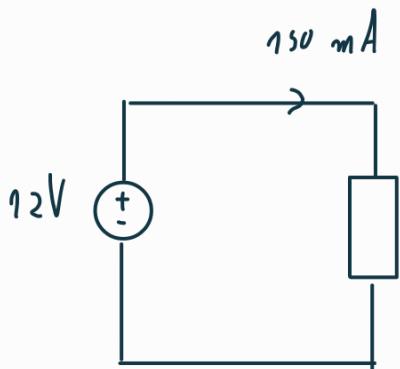7. A 12V car battery supplies a current of 150mA to a lightbulb. Find
- The power absorbed by the bulb
 - The energy absorbed by the bulb over an interval of 20 minutes



$$E = 1800 \cdot 20 \cdot 60 = 1800 \cdot 1200 = \dots$$

$$P = 1800 \text{ W}$$

8. A flashlight battery has a rating of 0.8 Ah and a lifetime of 10 hours. It has two batteries 3V in series. Find
- The current
 - Power P
 - Energy stored


$$\Rightarrow I = 0.08 \text{ A} \quad P = 0.08 \cdot 6 = 0.48 \text{ W} \quad E = 10 \cdot 60 \cdot 60 \cdot 0.48 =$$

9. A 30W light bulb is connected to a 120V source and is left on continuously in an otherwise dark staircase. Determine:
- The current through the lightbulb
 - The cost of operating the light for one (non-leap) year if electricity costs 12 cents per kWh.

$$I = \frac{P}{V} = \frac{30}{120} = \frac{1}{4} = 0.25 \text{ A} \quad P = 30 \text{ W} = 30 \cdot \frac{1000}{3600} \text{ kW h}$$

b) ...

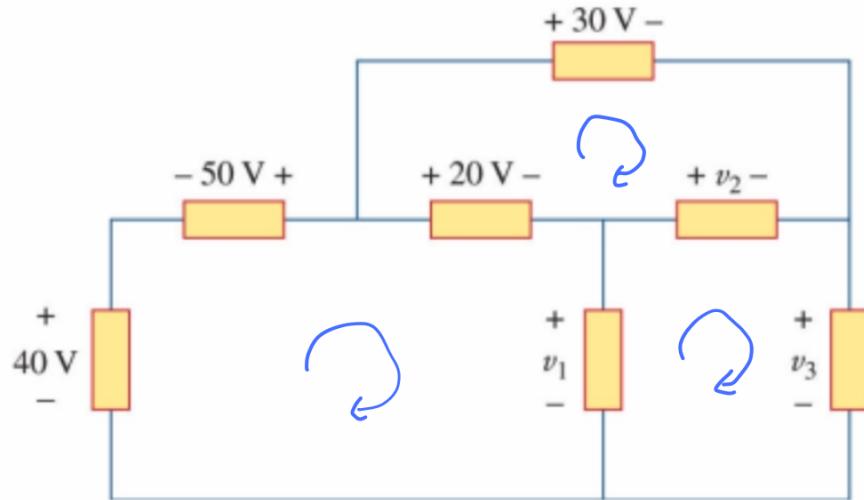10. Find v_1 , v_2 and v_3 in the circuit below





$$v_1 = -40 - 50 + 20 = -70 \text{ V}$$

$$v_2 = 30 - 20 = 10 \text{ V}$$

$$v_3 = 70 - 10 = 60 \text{ V}$$

Assignment 2

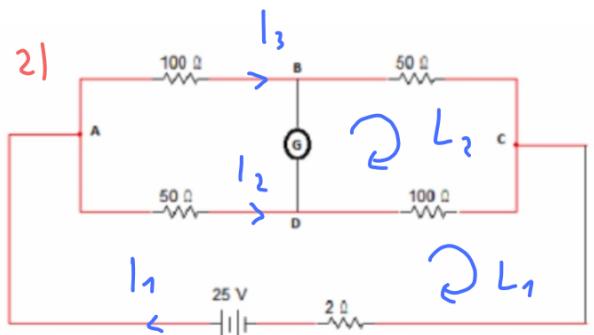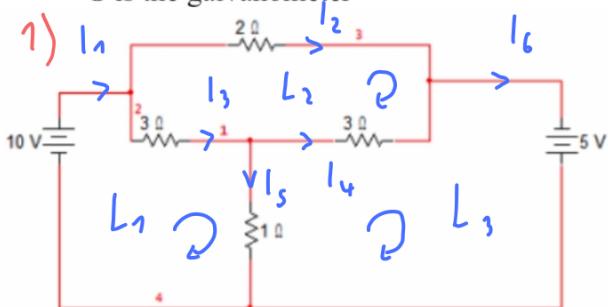1. Write KCL and KVL equations at node 1 (3 loops) and node A (2 loops) for the given circuits
G is the galvanometer



$$1) I_1 = I_2 + I_3$$

$$L_1: -10 + 3I_3 + I_5 = 0$$

$$I_3 = I_5 + I_4$$

$$L_2: 2I_2 - 3I_4 - 3I_5 = 0$$

$$I_2 + I_4 = I_6$$


$$L_3: -5 - I_5 + 3I_4 = 0$$

$$I_1 = I_5 + I_6$$

$$2) I_1 = I_2 + I_3, \quad L_1: -25 + 2I_1 + 50I_2 + 100I_3 = 0$$

$$L_2: 100I_3 + 50I_3 - 100I_2 - 50I_1 = 0$$

2. Given circuit below

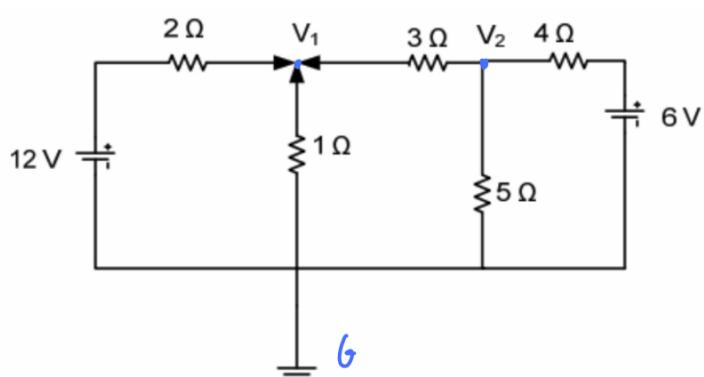


$$1: \frac{12 - V_1}{2} + \frac{V_2 - V_1}{3} - \frac{V_1}{1} = 0$$

$$2: \frac{6 - V_2}{4} - \frac{V_2 - V_1}{3} - \frac{V_2}{5} = 0$$

Find V_1 , V_2 and current passing through each resistor. 1 is a node among element 2, 3, and 1 Ω and 2 are a node among element 3, 4 and 5Ω

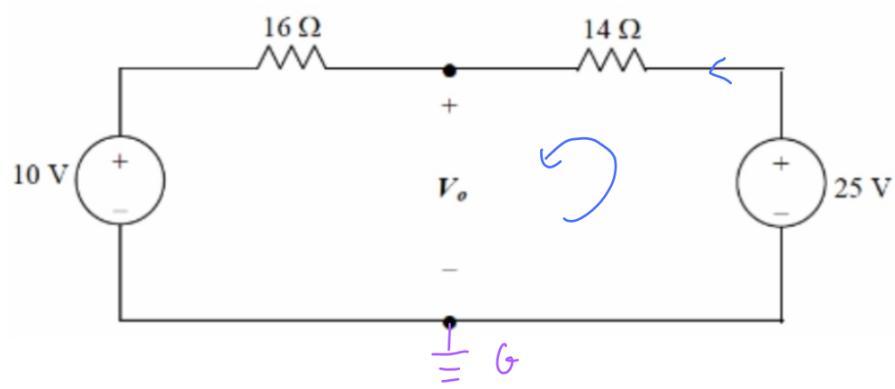
3. Given circuit below. Use KVL to determine V_o in the circuit



$$\begin{aligned} -25 + 10 + 14 &= 0 \Rightarrow \\ = -15 + 30 &= 15 = 0.5A \\ \Rightarrow V_o &= \end{aligned}$$

$$V_o = 25 + 0.5 \cdot 14 = 25 + 7 = 32$$

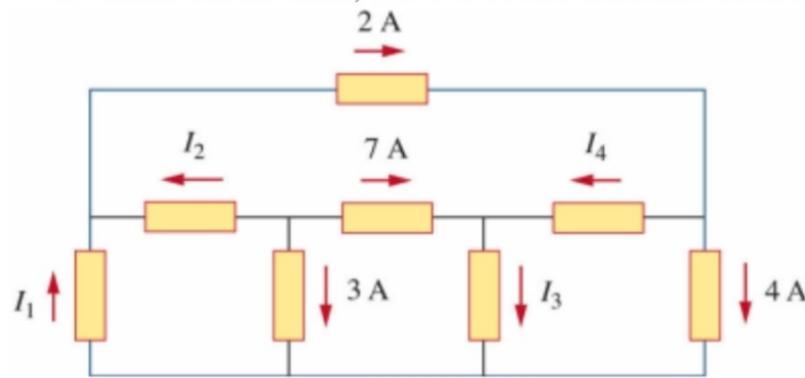4. For the circuit below, use KCL to find the branch current I_1 to I_4 :




$$2 - I_4 - 4 = 0 \Rightarrow I_2 = -2 A$$

$$7 + I_4 - I_3 = 1 \Rightarrow I_3 = 5 A$$

$$-I_2 - 7 - 3 = 0 \Rightarrow I_2 = -10 A$$


$$I_1 + I_2 = 2 \Rightarrow I_1 = 12$$

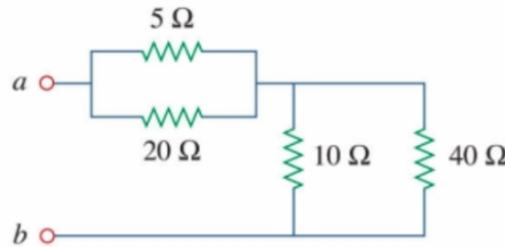5. Calculate the equivalent resistance, R_{ab} , at terminals a-b for the circuit below



$$R_{ab} = \frac{70\Omega}{25} + \frac{40\Omega}{50} = 4 + 8 = 12 \Omega$$

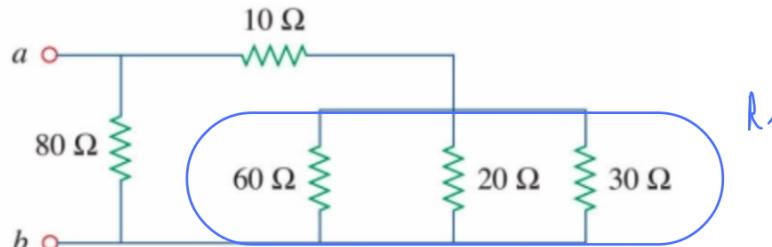
6. Calculate the equivalent resistance, R_{ab} , at terminals a-b for the circuit below



$$R_1 = \frac{1}{\frac{1}{60} + \frac{1}{20} + \frac{1}{30}} = \frac{1}{\frac{1+3+2}{60}} = 10 \Omega$$

$$R_{ab} = \frac{1600}{1600} = 16 \Omega$$

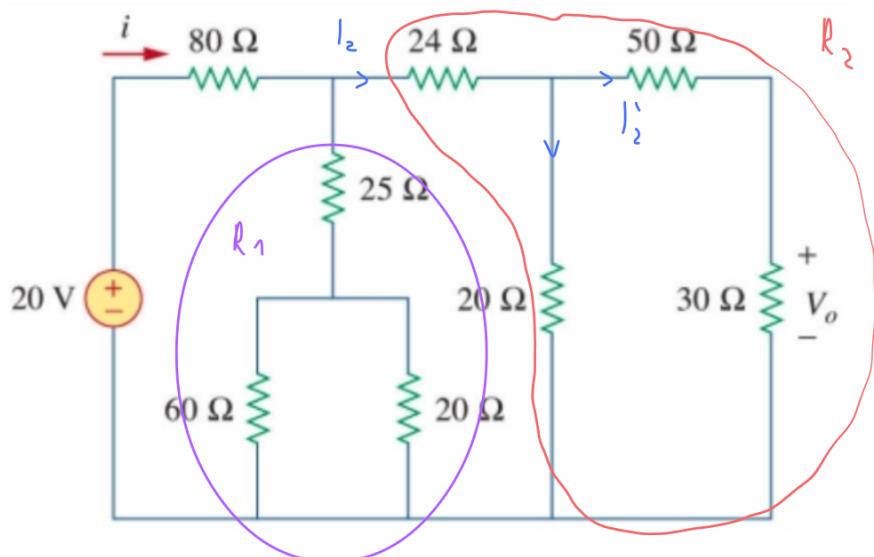7. Find i and V_o in the circuit below. This is to practice calculating R_{eq} for different purposes – first collapsing the circuit to a single R_{eq} value and then expanding it back out gradually to find V_o




$$R_1 = 25 + \frac{1200}{80} = 25 + 15 = 40 \Omega$$


$$R_2 = 24 + \frac{1600}{100} = 24 + 16 = 40 \Omega$$

$$R_{eq} = 80 + \frac{1600}{80} = 80 + 20 = 100 \Omega$$

$$= i = \frac{20}{100} = 0.2 A$$

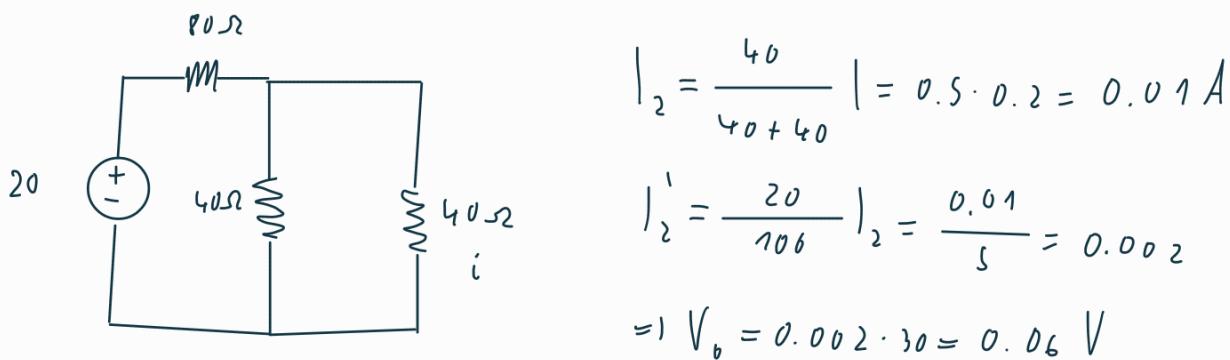

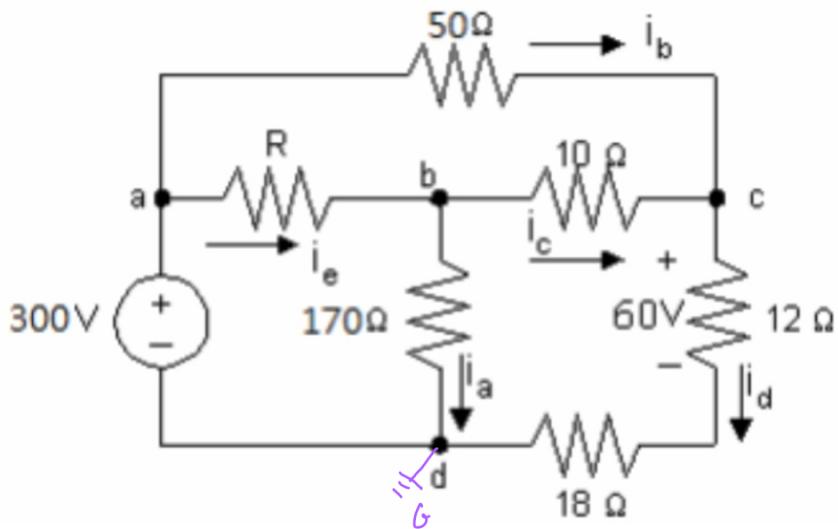8. Given circuit below. Find the value of R ?




$$i_d = \frac{60}{12} = 5 A \Rightarrow V_c = i_d \cdot (12 + 18) = 5 \cdot 30 = 150 V$$

$$i_b = \frac{300 - V_c}{50} = \frac{150}{50} = 3 A \Rightarrow i_c = 2 A$$

$$i_c = \frac{V_b - V_c}{10} = 20 = V_b - 150 \Rightarrow V_b = 170 V$$

$$i_a = \frac{V_b}{170} = 1 A \Rightarrow i_e = i_a + i_c = 3 A \Rightarrow R = \frac{300 - V_b}{i_e} = 3 A = 170 \Rightarrow R = \frac{170}{3} \Omega$$

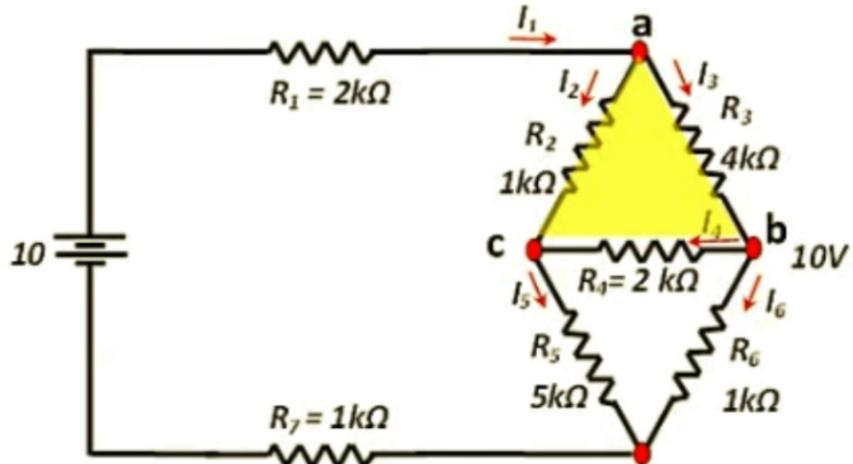9. Given circuit below. Find each current in the circuit



$$R_2' = \frac{1 \cdot 4}{1 + 4 + 2} = \frac{4}{7}$$

$$R_4' = \frac{2 \cdot 4}{7} = \frac{8}{7}$$

$$R_3' = \frac{2}{7}$$

$$R_5' = \frac{10}{8}$$


$$R_6' = \frac{2}{8}$$

$$R_7' = \frac{5}{8}$$

$$R_3' + R_5' = \frac{2}{7} + \frac{5}{4} = \frac{8 + 35}{28} = \frac{43}{28}$$


$$R = \frac{\frac{43}{28} \cdot \frac{39}{28}}{\frac{82}{28}} =$$

$$R_4' + R_6' = \frac{8}{7} + \frac{1}{4} = \frac{32 + 7}{28} = \frac{39}{28}$$

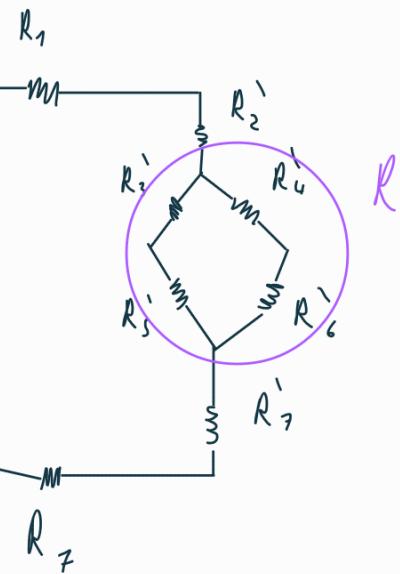

Assignment 3

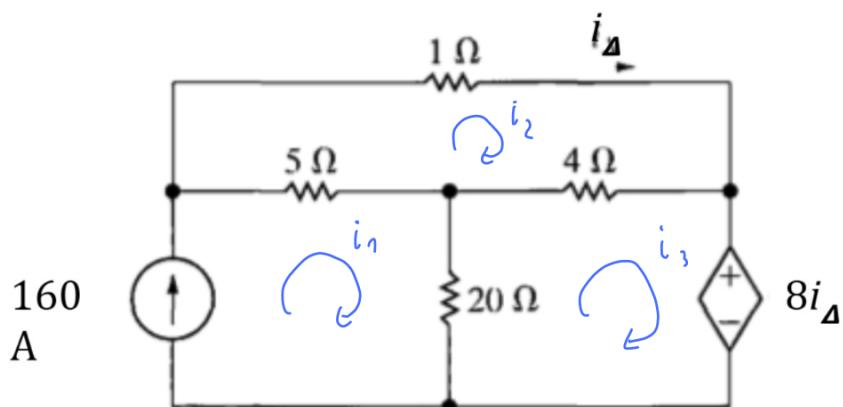1. The current source is 160 A and the current-controlled voltage source is $8i_A$. Use the **mesh-current method** to determine power on each element in the circuit



$$i_1 = 160 \text{ A}$$

$$i_2 = i_A$$

$$i_3 = ?$$


$$M_1: 160 + (i_1 - i_2)5 + (i_1 - i_3)20 = 0$$

$$M_2: 1 \cdot i_2 + (i_2 - i_3)4 + (i_2 - i_1)5 = 0$$

$$= 1 \quad \begin{cases} -5i_2 - 20i_3 = -160 \cdot 5 \\ 10i_2 - 4i_3 = 5 \cdot 160 \end{cases} = 1 \quad -44i_3 = -45 \cdot 160$$

$$= 1 \quad \begin{cases} 25 \cdot 160 - 5i_2 - 20i_3 = 0 \\ 10i_2 - 4i_3 - 5 \cdot 160 = 0 \end{cases}$$

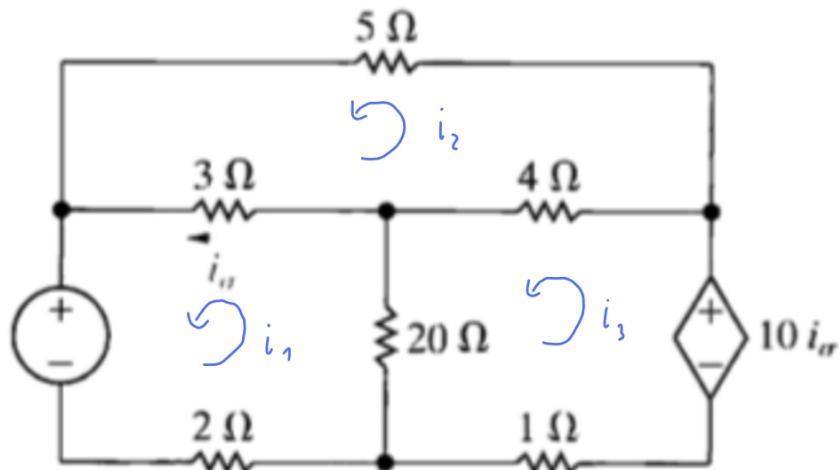2. The circuit is shown below. Use the **mesh-current method** to find the power extracted or dissipated by the current controlled voltage source.




$$M_1: 25i_1 - 3i_2 - 20i_3 + 225 = 0$$

$$M_2: -3i_1 + 12i_2 - 4i_3 - 10(i_1 - i_2) = 0$$

$$M_3: -20i_1 - 4i_2 + 25i_3 = 0$$

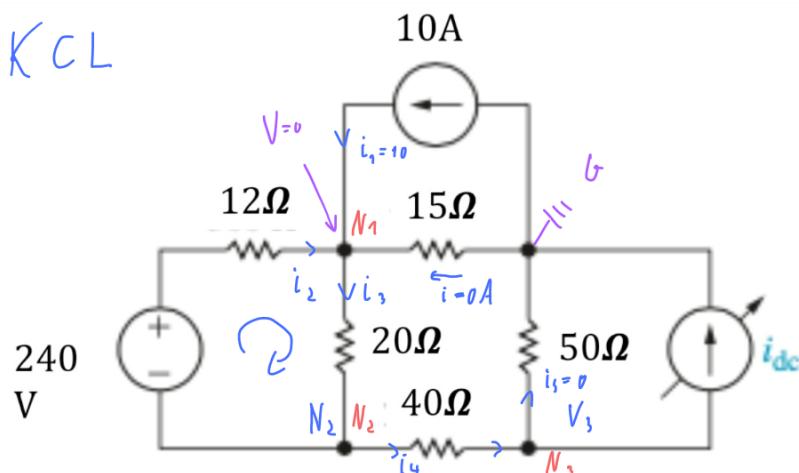3. The variable dc current source in the circuit below is adjusted so that the power developed by the 10A current source is zero. Find the value of i_{dc} .





$$N_1: 10 + \frac{V_2 + 240 - 0}{12} - \frac{0 - V_2}{20} + 0 = 0$$

$$N_2: \frac{V_2}{20} - \frac{V_2 + 240 - 0}{12} - \frac{V_2 - V_3}{40} = 0$$

$$N_3: \frac{V_2 - V_3}{40} - \frac{V_3 - 0}{50} - i_{dc} = 0$$

$$N_1 \Rightarrow V_2 = -225 \Rightarrow V_3 = -625 \Rightarrow i_{dc} = \frac{45}{2}$$

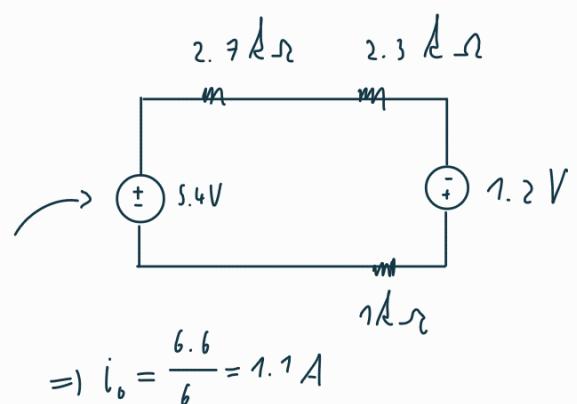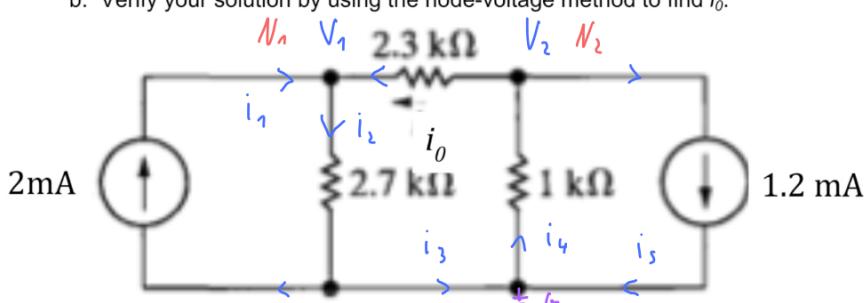4. The circuit is below
 a. Use a series of source transformations to find the current i_0 in the circuit.
 b. Verify your solution by using the node-voltage method to find i_0 .





$$b) i_1 = 2 \text{ mA} \quad i_3 = 1.2 \text{ mA}$$

$$\mathcal{N}_1: 2 + \frac{V_2 - V_1}{2.3} - \frac{V_1}{2.7} = 0$$


etc.

$$\mathcal{N}_2: \frac{0 - V_2}{1} - 1.2 - \frac{V_2 - V_1}{2.3} = 0$$

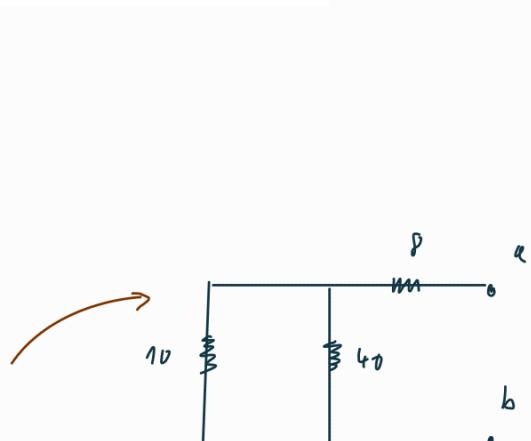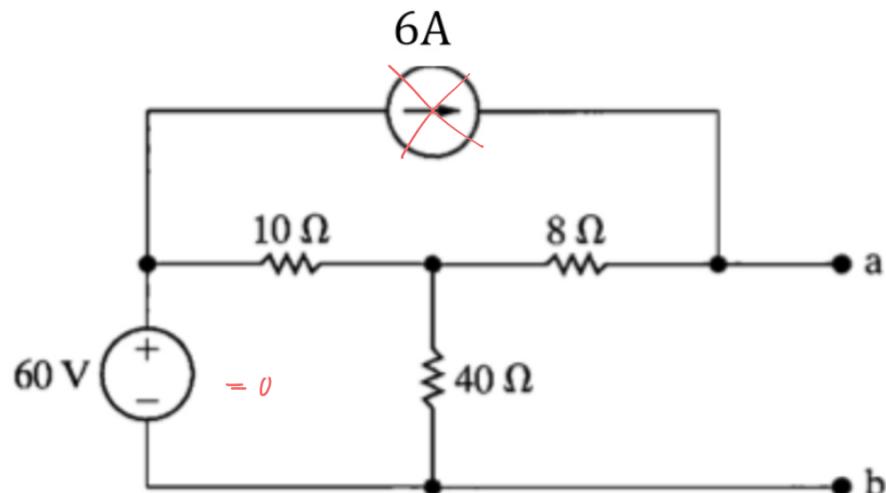5. The **current source is 6 A** is shown below. Find the Thévenin equivalent with respect to the terminals a, b for the circuit



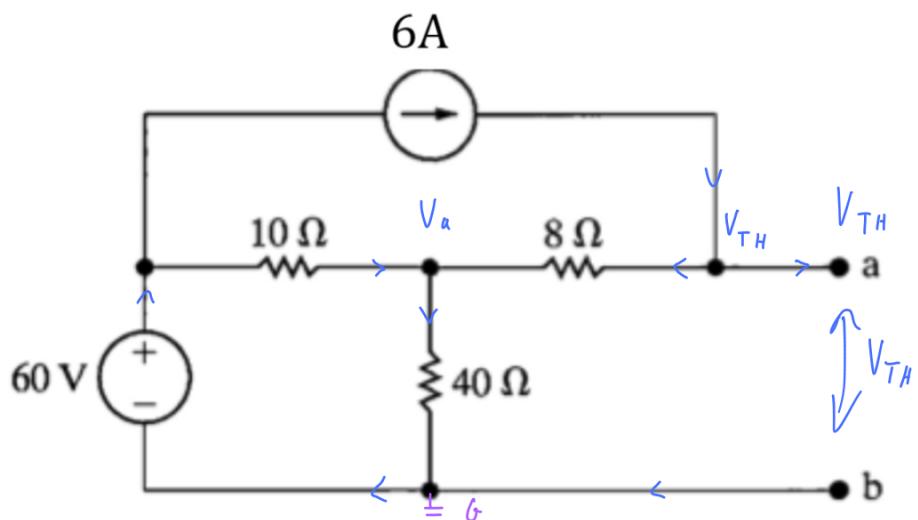
$$R_{TH} = \frac{40\Omega}{5\Omega} + R = 16\Omega$$



$$\left. \begin{aligned}
 & -\frac{V_{TH} - V_a}{8} + b = 0 \\
 & \frac{V_{TH} - V_a}{8} + \frac{60 - V_a}{10} - \frac{V_a}{40} = 0
 \end{aligned} \right\} \Rightarrow \begin{aligned}
 V_a &= \dots \\
 V_{TH} &= 144 \text{ V}
 \end{aligned}$$

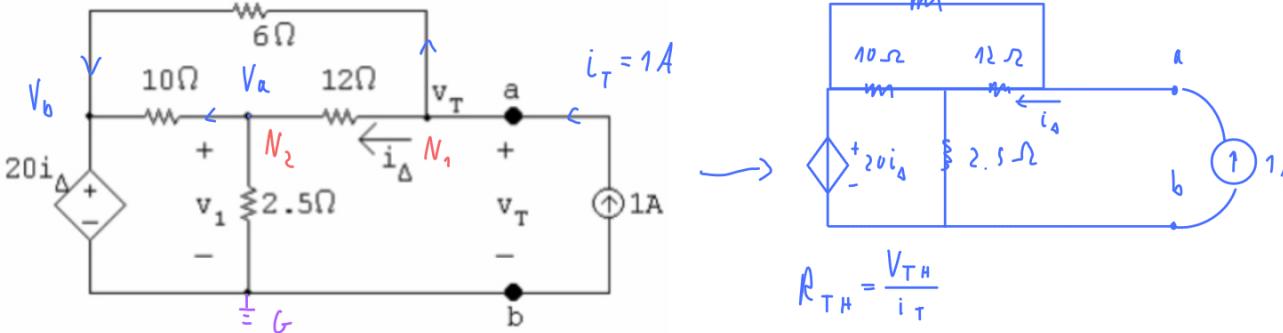6. The current controlled voltage source is $20i_A$. Find the Thévenin equivalent with respect to the terminals a, b for the circuit



$$i_A = \frac{V_{TH} - V_a}{12}$$

$$N_1: 1 - \frac{V_T - 20i_A}{6} - \frac{V_T - V_a}{12} = 0$$



$$N_2: \frac{V_T - V_a}{12} - \frac{V_a}{2.5} - \frac{V_a - 20i_A}{10} = 0$$

$\left. \begin{array}{l} \text{We know } i_A \\ = \end{array} \right\}$

$$\Rightarrow V_T = 27 \text{ V} \quad \text{and} \quad R_{TH} = 27 \text{ V}$$

7. The given circuit is below. The variable resistor in the circuit is adjusted for maximum power transfer to R_0

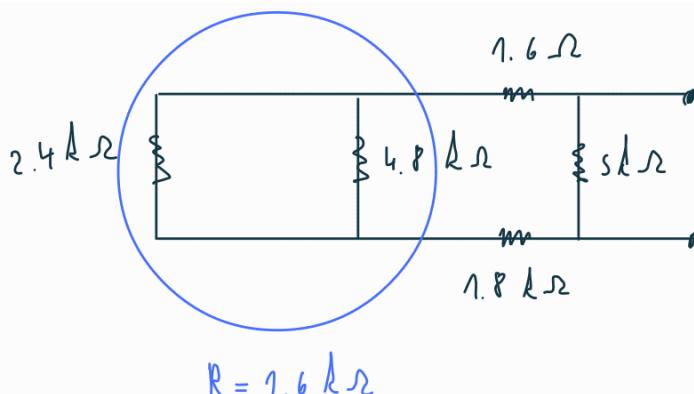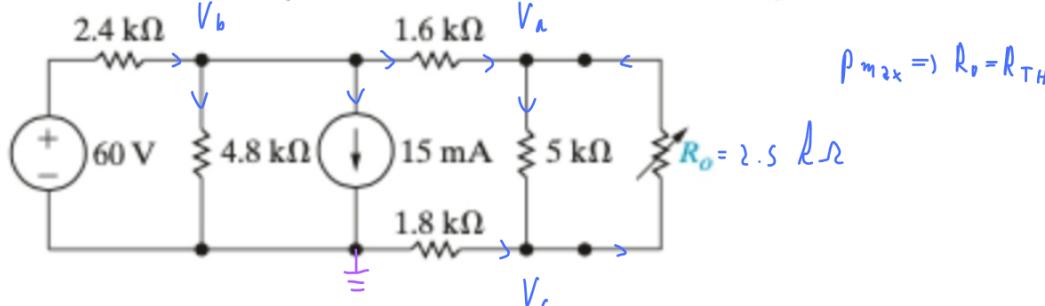- a. Find the value of R_0
 b. Find the maximum power that can be delivered to R_0



$$R_{TH} = 2.4 \text{ k}\Omega = R_0$$

$$N_a: \frac{V_c - V_a}{2.4} + \frac{V_b - V_a}{1.6} - \frac{V_a - V_c}{1.8} = 0$$

$$N_b: \frac{60 - V_b}{2.4} - \frac{V_b}{4.8} - 15 - \frac{V_b - V_c}{1.6} = 0$$

$$N_c: \frac{0 - V_c}{1.8} + \frac{V_a - V_c}{1.8} - \frac{V_c - V_a}{2.4} = 0$$


$$\Rightarrow \begin{cases} V_c = 4.32 \\ V_a = 8.32 \end{cases} \Rightarrow P = \frac{(V_c - V_a)^2}{R_0} = \frac{4^2}{2500} = \frac{16}{2500} = 0.064 \text{ W}$$

8. The variable resistor (R_0) in the circuit is adjusted until it absorbs maximum power from the circuit.


1. Find the value of R_0 .

2. Find the maximum power.

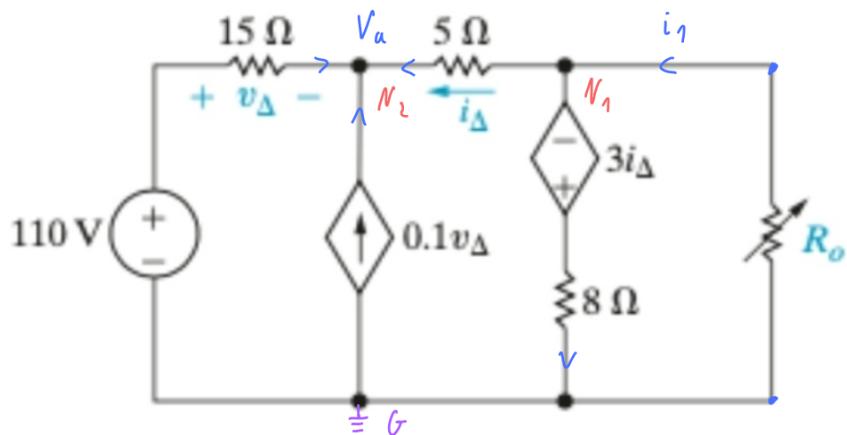3. Find the percentage of the total power developed in the circuit that is delivered to R_0 .


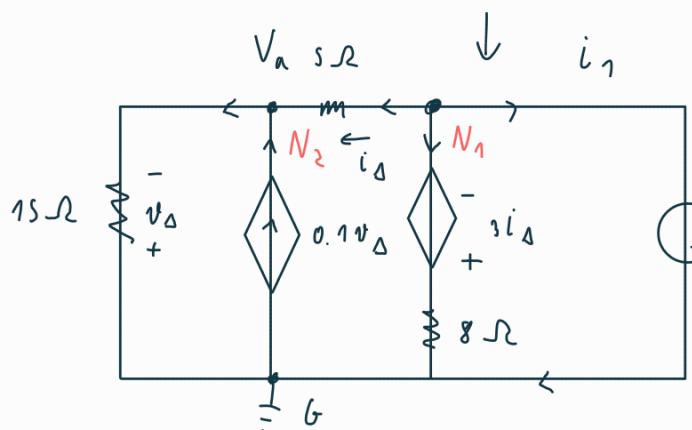
$$i_\Delta = \frac{1 - V_a}{s} = \frac{-0.2}{s} = -0.04$$




$$N_1: i_1 + \frac{1 + 3i_\Delta}{8} + i_\Delta = 0$$

$$N_2: \frac{-V_a}{15} + \frac{V_a}{10} + \frac{1 - V_a}{s} = 0 \quad | \cdot 30$$

$$\Rightarrow -2V_a + 3V_a + 6 - 6V_a = 0 \quad | : 5 \\ \Rightarrow V_a = 6 \quad | \quad V_a = 1.2V$$

$$i_1 = 0.04 - \frac{1 - 0.12}{8} = 0.04 - \frac{0.88}{8} = 0.04 - 0.11 = -0.07A$$
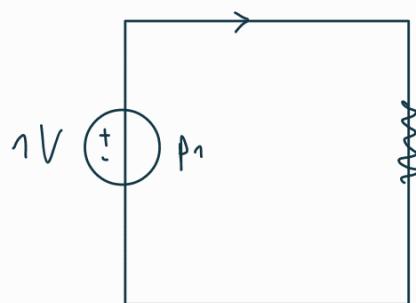
$$\frac{V_T}{i_T} = R_{TH} = R_0 = \frac{1}{0.07} = 14.28\Omega$$




$$P_1 = V \cdot I = 0.07$$

$$P_2 = I^2 \cdot R = I^2 \cdot \frac{1}{I} = I$$

2, 3 → back to the original ...

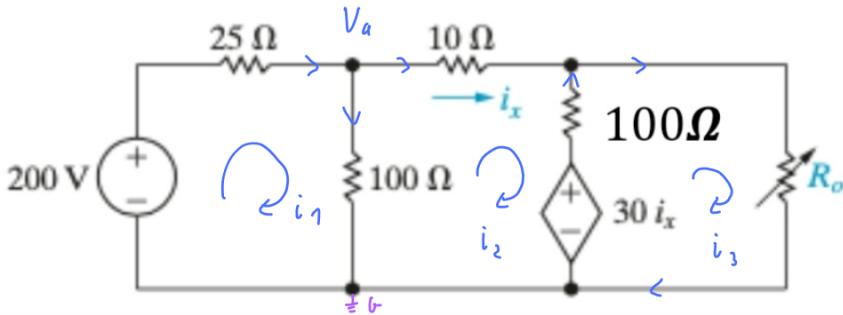9. The variable resistor (R_0) in the circuit below is adjusted until the power dissipated in the resistor is 225 W. Find the values of R_0 that satisfy this condition.




$$\begin{aligned} |^2 R &= 225 \rightarrow \\ \Rightarrow R &= \frac{225}{I^2} * \\ \Rightarrow I &= \frac{\pm 15}{\sqrt{R}} \end{aligned}$$

$$\left\{ \begin{array}{l} -200 + 25i_1 + 100i_1 - 100i_2 = 0 \\ 10i_2 + 100(i_2 - i_3) + 30i_2 + 100(i_2 - i_1) = 0 \\ 100(i_3 - i_2) + i_3 R_0 - 30i_2 = 0 \quad (*) \Rightarrow 100(i_3 - i_2) + 225i_3 - 30i_2 = 0 \\ \bullet \quad i_1 = \frac{8}{3} \quad i_2 = \frac{4}{3} \quad i_3 = \frac{8}{15} \quad \Rightarrow R = \frac{225}{\frac{8}{15}} = \frac{1}{8} = 0.125 \Omega \end{array} \right.$$

10. In the circuit below, before the 5 m A current source is attached to the terminals a, b, the current i_0 is calculated and found to be 3.5 mA.

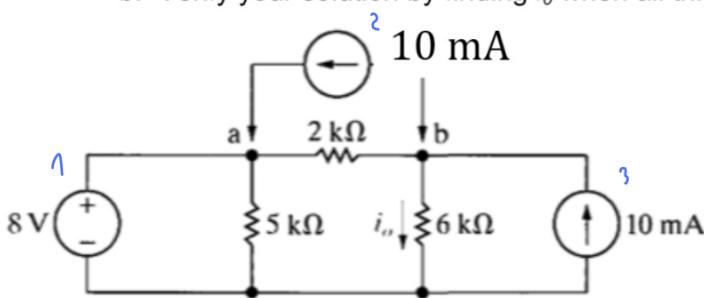- a. Use superposition to find the value of i_0 after the current source is attached.
b. Verify your solution by finding i_0 when all three sources are acting simultaneously.



$$1) R_{eq} = \frac{5 \cdot 8}{13} = \frac{40}{13} \Rightarrow V = \frac{6}{8} \cdot 8 = 6 \quad i_0' = \frac{6}{6} = 1$$

$$2) R_{eq} = \frac{2 \cdot 11}{13} = \frac{22}{13} \Rightarrow i_0'' = 10 \cdot \frac{2}{13} = \frac{20}{13} \quad i_0 = i_0' + i_0'' + i_0''' = \frac{10}{13} + 1 = \frac{27}{13}$$


$$3) i_0''' = 10 \cdot \frac{7}{13} = \frac{70}{13}$$

Assignment 4

$$\frac{1}{jwC} \quad \frac{1}{j} = -j$$

1. The two circuits are below

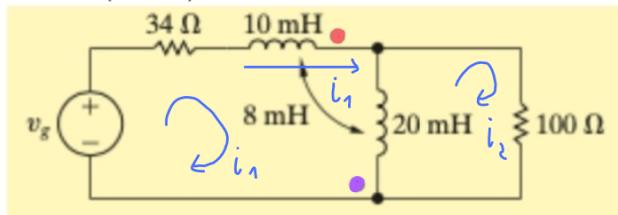- a. Find the average power delivered to the 100Ω resistor in the circuit shown if $v_g = 660\cos(5000t)$ V.



$$10 \text{ mH} \rightarrow jwL = s \cdot 10 \cdot 10^{-3} = 50j \Omega$$

$$20 \text{ mH} \rightarrow 100j \Omega$$

$$8 \text{ mH} \rightarrow 40j \Omega$$

in which dot
induced by

$$\begin{cases} -10j + 34i_1 + 50j i_1 + 100j(i_1 - i_2) + 40j(i_1 - i_2) + 40j i_1 = 0 \\ 100j(i_2 - i_1) + 100i_2 - 40j i_1 = 0 \end{cases} (=)$$

$$v_f = A \cos(w \cdot t + \theta) = A \cdot (\cos \theta + j \sin \theta) = 660 \cdot (1 + 0 \cdot j) = 660$$

$$A e^{j\theta} = A \cos(wt + \theta)$$

i_1 pleacă $\rightarrow p+$

$$a + bj = A e^{j\theta} = A < \theta$$

$\rightarrow i_-$

$$A = \sqrt{a^2 + b^2}$$

i_1 intră $\rightarrow p-$

$\rightarrow i_+$

$$\theta = \arctan \frac{b}{a}$$

$$= \begin{cases} 34i_1 + 230j i_1 - 140j i_2 = 660 \\ -140j i_1 + 100i_2 + 100j i_2 \end{cases} \quad i_1 = \frac{100(1+j)}{140} i_2$$

$$= \frac{34 \cdot 100(1+j)}{140} i_2 + \frac{230j \cdot 100 \cdot (1+j)}{140} i_2 - 140j i_2 = 660$$

$$= \frac{3400(1+j)}{140} i_2 + \frac{23000j(1+j)}{140} i_2 - 140j i_2 / 140$$


$$= 3400i_2 + 3400j i_2 + 23000j i_2 - 23000i_2 - 19600j i_2 = 660 \quad \rightarrow$$

$$= -19600i_2 + 6800j i_2 = 660 \quad \rightarrow \frac{1}{i_2} = \frac{4900 + 1700j}{660}$$

$$= -19600 + 6800j = \frac{660}{i_2} \quad \rightarrow i_2 = \frac{660}{-19600 + 6800j} = \frac{165}{-4900 + 1700j} = \frac{808500 + 280500j}{4900^2 - 1700^2} =$$

$$= \frac{808500 + 280500j}{21120000} \cup = \frac{8085 + 2805j}{211200} = \frac{1117 + 561j}{42240} \quad P = \frac{1}{2} \cdot i_2^2 \cdot R$$

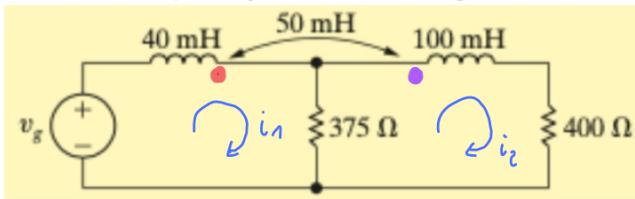- b. Find the average power delivered to the 400Ω resistor in the circuit shown if $v_g = 248\cos(10,000t)$ V. Find the average power delivered to the 375Ω resistor. Find the power developed by the ideal voltage source.



$$\begin{aligned} jwL \\ 40 \text{ mH} &\rightarrow 40 \cdot 10^{-3} \cdot 10^4 = 400j \\ 50 \text{ mH} &\rightarrow 50 \cdot 10^{-3} \cdot 10^4 = 500j \\ 100 \text{ mH} &\rightarrow 100 \cdot 10^{-3} \cdot 10^4 = 1000j \end{aligned}$$

$$v_f = 248 \cos(10,000t) = 248(\cos \theta + j \sin \theta) = 248$$

$$\left\{ \begin{array}{l} 400j i_1 + 37s(i_1 - i_2) - 500j i_2 = 248 \\ 1000j i_2 + 400i_2 + 37s(i_2 - i_1) - 500j i_1 = 0 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} (37s + 400j)i_1 + (-37s - 500j)i_2 = 248 \\ (37s + 1400j)i_2 + (-37s - 500j)i_1 = 0 \end{array} \right.$$

$$= 1 \quad i_1 = \dots \quad i_2 = \dots \quad P_{37s} = \frac{1}{2} (i_1 - i_2)^2 \cdot 37s =$$

$$P_{v_f} = V \cdot I ?$$

$$\begin{aligned} A e^{j\theta} &= A \angle \theta = A \cos(wt + \theta) = \\ &= A (\cos \theta + j \sin \theta) \end{aligned}$$


2. The circuit is below

- a) Find the steady-state expression for the currents i_g and i_L in the circuit when $v_g = 168\cos(800t)$

V

- b) Find the coefficient of coupling k .

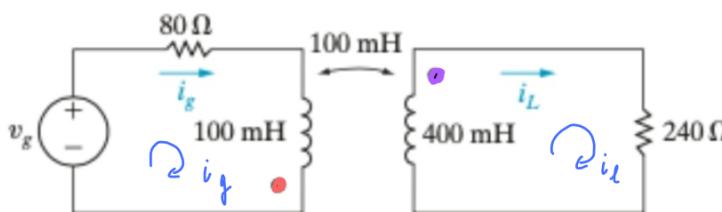- c) Find the energy stored in the magnetically coupled coils at $t = 625\pi \mu s$ and $t = 1250\pi \mu s$.




$$\begin{aligned} jwL \\ 100 \text{ mH} &\rightarrow 100 \cdot 10^{-3} \cdot 8 \cdot 10^2 = 80j \\ 400 \text{ mH} &\rightarrow 400 \cdot 10^{-3} \cdot 8 \cdot 10^2 = 320j \end{aligned}$$


$$\begin{aligned} k &= \frac{M}{\sqrt{L_1 \cdot L_2}} = \\ &= \frac{100 \text{ mH}}{\sqrt{40000 \text{ mH}}} = \\ &= \frac{1}{2} \end{aligned}$$

$$\begin{aligned} v_f &= 168 \cos(800t) = 168(\cos \theta + j \sin \theta) = 168 \quad \left| \begin{array}{l} 10(1+j) i_g + 10j i_L = 21 \\ \Rightarrow i_L = -0.3(1+6j) \Rightarrow i_g = 0.3(22-3j) \end{array} \right. \\ \left\{ \begin{array}{l} 80i_g + 80j i_g + 80j i_L = 168 \\ 240i_L + 320j i_L + 80j i_g = 0 \end{array} \right. &\Rightarrow \left\{ \begin{array}{l} 20i_g + 20j i_g + 20j i_L = 42 \\ 3i_L + 4j i_L + j i_g = 0 \end{array} \right. \quad \left| \begin{array}{l} \frac{1}{j} \\ \frac{1}{j} \end{array} \right. \Rightarrow \frac{3}{j} i_L + 4i_L + i_g = 0 = \\ &\Rightarrow 3j i_L + 4i_L = -i_g \Rightarrow i_g = -(4+3j)i_L \end{aligned}$$

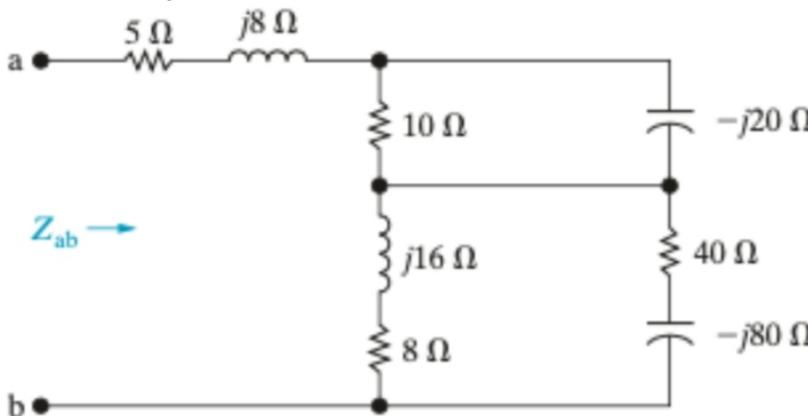4. Find the impedance Z_{ab} in the circuit




$$Z_{ab} \rightarrow$$

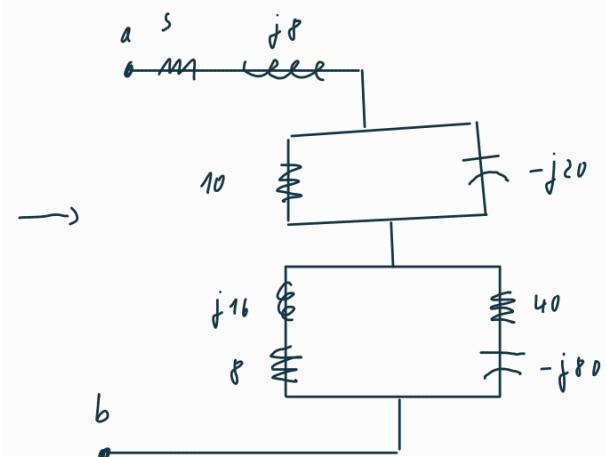

$$\begin{aligned}
 Z_{ab} &= s + 8j + \frac{(-200j)}{10(1+2j)} + \frac{8(1+2j) \cdot 40 \cdot (1-2j)}{48 - 64j} = s + 8j - \frac{20j}{1+2j} + \frac{320(1+4)}{3-4j} = \\
 &= s + 8j - \frac{20j - 40}{s} + \frac{300 + 400j}{2s} = \frac{62s + 200j - 100j + 200 + 300 + 400j}{2s} = \frac{112s + 500j}{2s} = 4s + 20j
 \end{aligned}$$

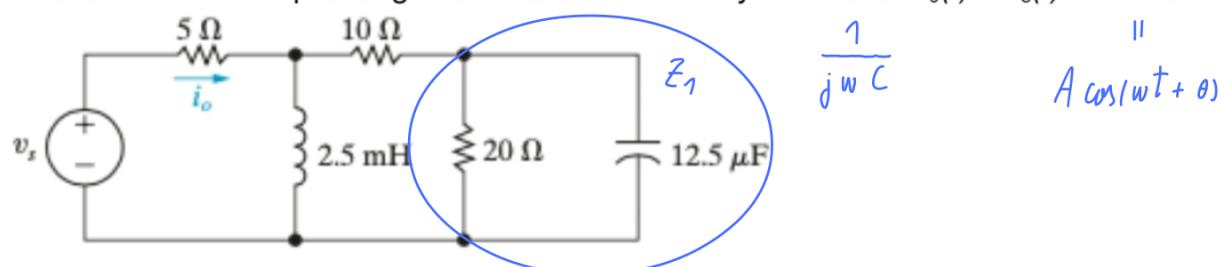5. The circuit is operating in the sinusoidal steady state. Find $i_0(t)$ if $v_s(t) = 25 \sin 4000t$ V.



$$2.5 \text{ mH} \rightarrow 2.5 \cdot 10^{-3} \cdot 4 \cdot 10^3 = 10j$$


$$12.5 \mu\text{F} \rightarrow \frac{1}{j \cdot 4 \cdot 10^3 \cdot 12.5 \cdot 10^{-6}} = \frac{1}{50j \cdot 10^{-3}} = \frac{1}{5} \cdot 10^2 \cdot \frac{1}{j} = -20j$$

$$Z_1 = \frac{20 \cdot (-20j)}{20(1-j)} = \frac{-20j}{1-j} = \frac{-20j + 20}{2} = 10 - 10j$$

$$Z_{eq} = \frac{(20 - 10j) \cdot 10j}{20 - 10j + 10j} = \frac{200j - 100 + s}{20} = -s + 10j + s = 10j$$

$$\begin{aligned}
 I = \frac{V}{Z} &= \frac{25 \cos(4000t)}{10j} = \frac{5}{2}(-j) \cos(4000t) = (-j) \cdot \frac{5}{2}(\cos 90^\circ + j \sin 90^\circ) = (-j) \frac{5}{2} \cdot 1 = -\frac{5}{2}j = \\
 &= -\frac{5}{2}(\cos 90^\circ + j \sin 90^\circ) = -\frac{5}{2}\cos(4000t + \frac{\pi}{2}) =
 \end{aligned}$$

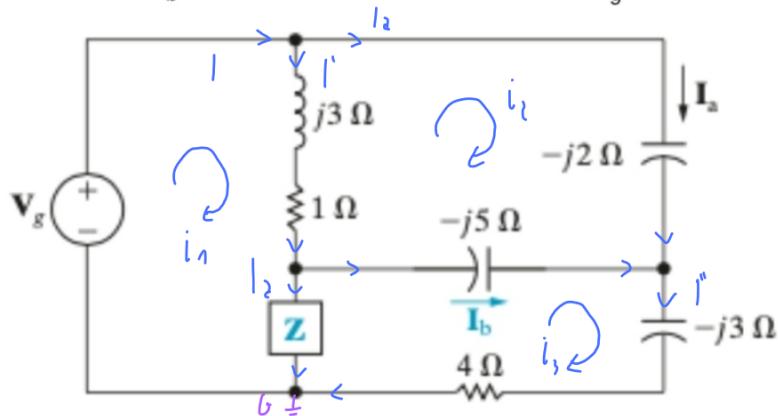6. Find I_b and Z in the circuit below if $V_g = 25 \angle 0^\circ$ V and $I_a = 5 \angle 90^\circ$ A.



$$V_g = 25 \angle 0^\circ = 25 \cos(t + 0^\circ) = 25 (\cos 0^\circ + j \sin 0^\circ) = 25$$

$$i_1 = I_a = 5 \angle 90^\circ = 5 \cos(t + 90^\circ) = 5 (\cos 90^\circ + j \sin 90^\circ) = 5j$$

$$M_1: 3j(i_1 - i_2) + i_1 - i_2 + Z(i_1 - i_3) = V_g$$


$$M_2: 3j(i_2 - i_1) - 2j i_2 - 5j(i_2 - i_3) + i_2 - i_1 = 0$$

$$M_3: -5j(i_3 - i_2) - 3j i_3 + 4i_3 + Z(i_3 - i_1) = 0$$

$$\Rightarrow \begin{cases} 3j i_1 + i_1 - 5j + Z i_1 - 2i_3 = 10 \\ -15 - 3j i_1 + 10 + 2s - 5j i_3 + 5j - i_1 = 0 \\ -5j i_3 - 2s - 3j i_3 + 4i_3 + Zi_3 - Zi_1 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} (1+3j+Z)i_1 + (-2)i_3 = s(2+j) \\ (-1-3j)i_1 + (-5j)i_3 = -s(4+j) \\ (-Z)i_1 + (4-8j+Z)i_3 = 2s \end{cases}$$

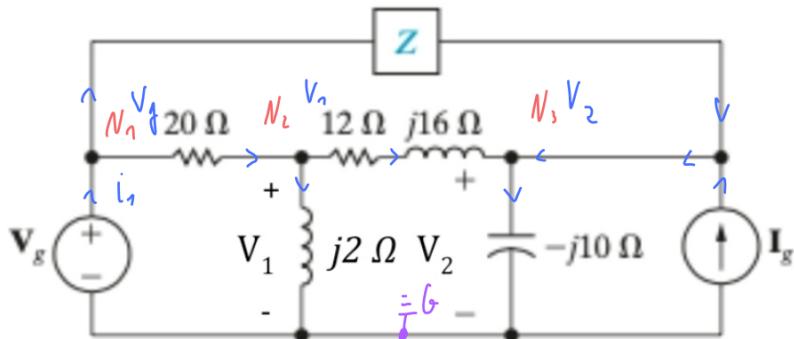7. Find the value of Z in the circuit, if $V_g = 100 - j50$ V, $I_g = 30 + j20$ A, and $V_1 = 140 + j30$ V.



$$N_1: i_1 - \frac{V_g - V_1}{20} - \frac{V_1 - V_2}{Z} = 0$$

$$i_1 - \frac{-40 - 80j}{20} + \frac{100 - 50j - V_2}{Z} = 0$$

$$N_2: \frac{V_g - V_1}{20} - \frac{V_1 - V_2}{4(3+4j)} - \frac{V_1}{2j} = 0 \quad \Rightarrow$$

$$(1) N_3: \frac{V_1 - V_2}{4(3+4j)} - \frac{V_2}{(-j10)} + \frac{V_1 - V_2}{Z} + j = 0$$

$$\frac{-40 - 80j}{20} - \frac{140 + 30j - V_2}{4(3+4j)} - \frac{140 + 30j}{2j} = 0 \quad \Rightarrow -2 - 4j - 70 - 15j = \frac{140 + 10j - V_2}{4(3+4j)} \quad \Rightarrow$$



$$\Rightarrow (-72 - 19j)4(3+4j) = 140 + 30j - V_2 \quad \Rightarrow$$

$$\Rightarrow -4(-72 - 11j)(3+4j) + 140 + 30j = V_2 \quad \Rightarrow V_2 = 700 + 1410j$$

$$N_3: \frac{140 + 30j - 700 - 1410j}{4(3+4j)} + \frac{700 + 1410j}{10j} + \frac{100 - 50j - 700 - 1410j}{Z} + 30 + 20j = 0$$

$$\Rightarrow Z = -90 - 576j$$

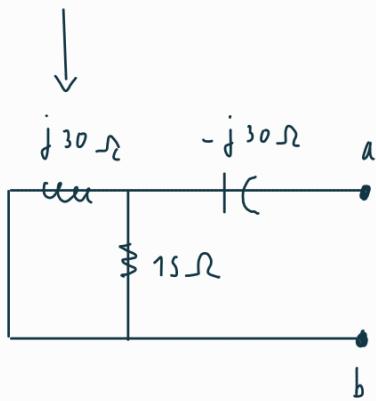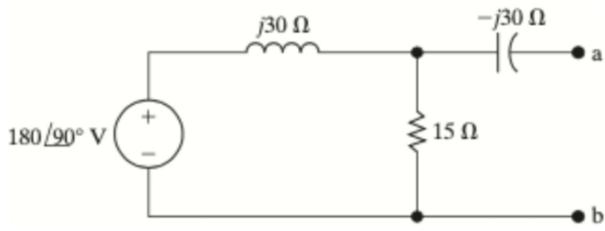8. Use source transformations to find the Norton equivalent circuit with respect to the terminals a,b for the circuit




$$\begin{aligned}
 Z_{eq} &= -30j + \frac{2 \cdot 15^2 \cdot j}{1s + 30j} = \cancel{-30j} + \cancel{\frac{900j}{1s + 30j}} \\
 &= -30j + \frac{450j}{1s(1+2j)} = -30j + \frac{30j}{1+2j} = \\
 &= -30j + \frac{30j + 60}{5} = -30j + 6j + 12 = \\
 &= 12 - 24j = 12(1 - 2j)
 \end{aligned}$$

best bet:

$$i_N = \frac{V}{R_N} = \frac{180 \angle 90^\circ}{12(1-2j)} = \frac{15(4\angle 90^\circ + j \sin 90^\circ)}{1-2j} = \frac{15j - 30}{s} = -6 + 3j = -3(2-j)$$

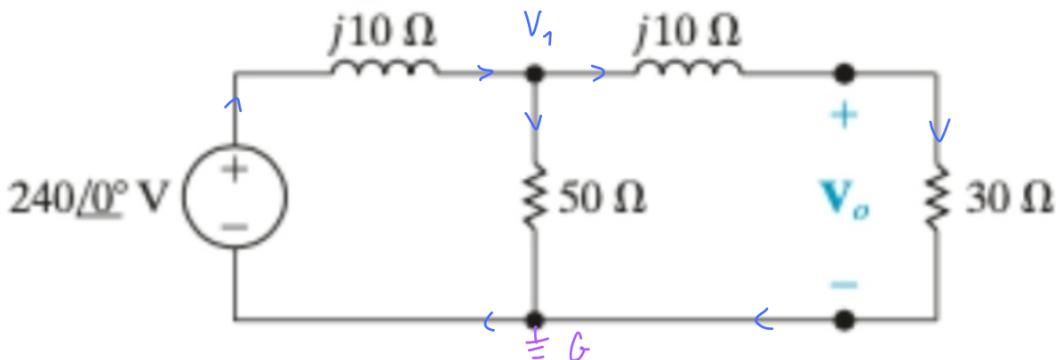9. Use the node-voltage method to find V_o in the circuit:



$$240 \angle 0^\circ = 240$$

$$\frac{240 - V_1}{10j} - \frac{V_1}{30 + 10j} - \frac{V_1}{50} = 0 \Rightarrow \frac{240 - V_1}{10} (-j) - \frac{V_1}{10(3+j)} - \frac{V_1}{50} = 0 \Rightarrow$$

$$\Rightarrow \frac{-240j + V_1 j}{10} - \frac{(3-j)V_1}{10 \cdot 4} - \frac{V_1}{50} = 0 \quad / \cdot 200 \Rightarrow$$

nimrod


$$\Rightarrow -4800j + 20jV_1 - 50(3-j)V_1 - 40V_1 = 0 \Rightarrow$$

$$\Rightarrow 20jV_1 - 150V_1 + 50jV_1 - 40V_1 = 4800j \Rightarrow 7j + 19V_1 = 4800j$$

$$\Rightarrow V_1(-190 + 70j) = 4800j \Rightarrow V_1 = \frac{4800j}{-190 + 70j} = \frac{480j}{-19 + 7j} = \frac{336}{41} - \frac{912}{41}j$$

$$V_o = V_1 \cdot \frac{30}{30+10j} = V_1 \cdot \frac{3}{3+j} = \frac{9-3j}{4} \cdot V_1 = \frac{29}{41} - \frac{922}{41}j$$

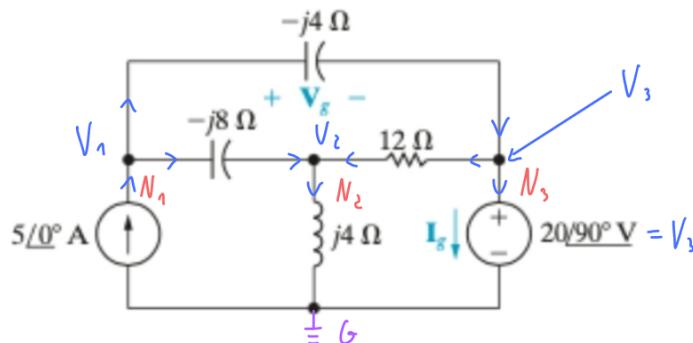10. Use the node-voltage method to find the phasor voltage V_g in the circuit




$$S \angle 0^\circ A = S(\cos 0^\circ + j \sin 0^\circ) = S \cdot (1 + j \cdot 0) = S$$

$$20 \angle 90^\circ V = 20(\cos 90^\circ + j \sin 90^\circ) = 20(0 + j \cdot 1) = 20j = V_3$$

$$\begin{aligned} N_1: \quad & S - \frac{V_1 - V_3}{-4j} - \frac{V_1 - V_2}{-8j} = 0 \\ N_2: \quad & \frac{V_1 - V_2}{-8j} + \frac{V_3 - V_2}{12} - \frac{V_2}{4j} = 0 \\ \left(N_3: \quad & \frac{V_1 - V_3}{-4j} - \frac{V_3 - V_2}{12} = 0 \right) \end{aligned} \quad \left. \begin{array}{l} V_1 = \frac{-20}{3} \\ V_2 = \dots \text{not needed} \end{array} \right\} \Rightarrow V_g = V_1 - V_3 = \frac{-20}{3} + 20j = \frac{-20 + 60j}{3} = \frac{-20(1 - 3j)}{3}$$

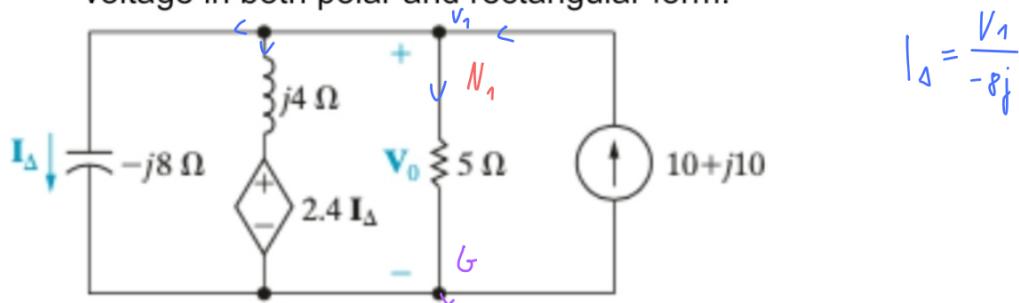11. Use the node-voltage method to find the phasor voltage V_o in the circuit. Express the voltage in both polar and rectangular form.



$$I_A = \frac{V_1}{-8j}$$


$$\frac{1}{j} = -j$$

$$N_1: 10 + j10 - \frac{V_1}{5} - 2.4 I_A - \frac{V_1}{-8j} = 0 \Rightarrow 10(1+j) - \frac{V_1}{5} + 2.4 \frac{V_1}{8j} + \frac{V_1}{8j} = 0 \Rightarrow$$

$$\Rightarrow 10(1+j) - \frac{V_1}{5} + \frac{3V_1}{10} + \frac{V_1}{8j} = 0 / 40 \Rightarrow 400(1+j) - 8V_1 + 12V_1 - 5V_1 = 0$$

$$\Rightarrow V_1 = -400(1+j) = -400 \cdot \sqrt{2} e^{j45^\circ}$$

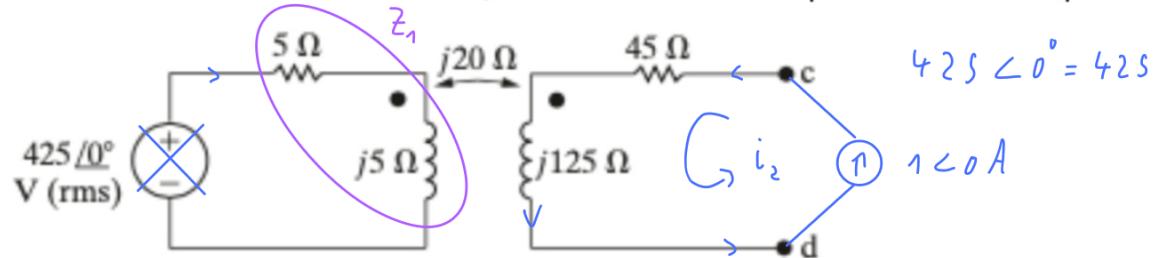
12. For the circuit below, find the Thévenin equivalent with respect to the terminals c,d



$$Z_{th} = (45 + 12s_j) + Z_r \quad ; \quad Z_r = \left(\frac{wM}{|Z_1|}\right)^2 \cdot Z_1^* = \left(\frac{w \cdot 20j}{s\sqrt{2}}\right)^2 \cdot (s - s_j) = ???$$

W not known

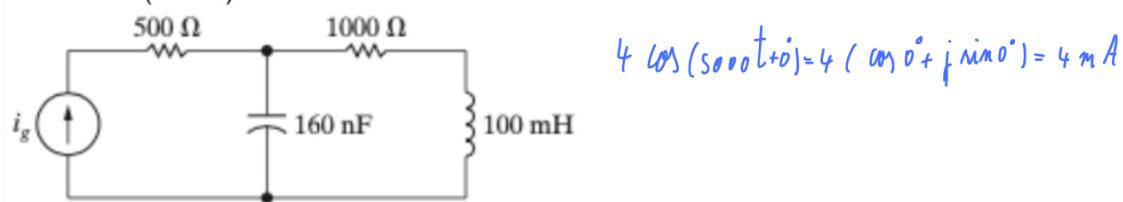13. Find the average power delivered by the ideal current source in the circuit below if $i_g = 4\cos(5000t)$ mA.



$$Z_c = \frac{1}{jwC} = \frac{1}{j \cdot 5 \cdot 10^{-3} \cdot 160 \cdot 10^{-9}} = \frac{1}{j 800 \cdot 10^{-6}} = \frac{-j}{8 \cdot 10^{-4}} = -j \cdot 0.125 \cdot 10000 = -1250j$$

$$Z_L = jwL = j \cdot 5 \cdot 10^{-3} \cdot 100 \cdot 10^{-3} = 500j$$


$$Z_{eq} = \frac{(1000 + 500j) \cdot (-1250j)}{1000 - 750j} + 500 = \frac{-500(2+j) \cdot 1250j}{250(4-j)} + 500 = \frac{-2(2j-1) \cdot 1250}{4-j} + 500 =$$

$$= \frac{-2(8j - 4 - 6 - 3j) \cdot 1250}{25} + 500 = \frac{-2(-10 + 5j) \cdot 10 \cdot 25 \cdot 5}{25} + 500 =$$

$$= -100(-10 + 5j) + 500 = 1000 - 500j + 500 = 500(3 - j)$$

$$V = i_g \cdot Z_{eq} = 4 \cdot 10^{-3} \cdot 5 \cdot 10^2 \cdot (3 - j) = 2(3 - j) \quad P = \frac{1}{2} |V| \cdot |I| = \frac{1}{2} \cdot 2 \cdot (3 - j) \cdot 4 \cdot 10^{-3} = 4(3 - j) \cdot 10^{-3}$$

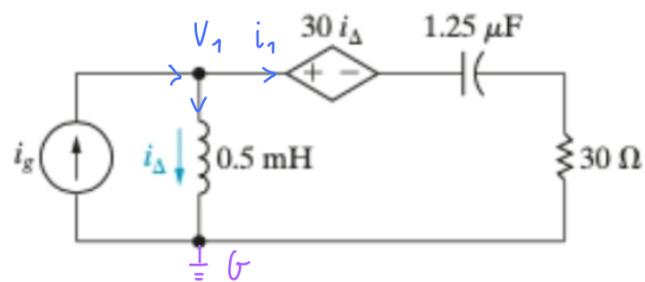14. Find the average power dissipated in the $30\ \Omega$ resistor in the circuit if $i_g = 6\cos(20,000t)$ A. = 6 V



$$0.5\text{ mH} \rightarrow \frac{1}{2} \cdot 10^{-3} \cdot 2 \cdot 10^4 = 10\text{ j}\Omega$$

$$1.25\text{ } \mu\text{F} \rightarrow \frac{1}{j \cdot 1.25 \cdot 10^{-6} \cdot 2 \cdot 10^4} = \frac{-j}{2.5 \cdot 10^{-2}} = -j \cdot 100 \cdot 0.4 = -40\text{ j}$$

$$6 - \frac{V_1}{10\text{j}} - \frac{V_1 + 30i_A}{-40\text{j} + 30} = 0 \quad (=) \quad 6 + \frac{V_1\text{j}}{10} - \frac{V_1 - 3\text{j}V_1}{-40\text{j} + 30} = 0 \quad (=)$$

$$i_A = \frac{V_1}{10\text{j}} = \frac{-V_1\text{j}}{10} \quad (=) \quad 6 + \frac{V_1\text{j}}{10} - \frac{V_1(1 - 3\text{j})}{10(3 - 4\text{j})} = 0 \quad / \cdot 10 \quad (=)$$

$$30 \frac{V_1}{10\text{j}} = \frac{3V_1}{\text{j}} = -3\text{j}V_1 \quad (=) \quad 60 + V_1\text{j} - \frac{V_1(3 - 4\text{j} + 4\text{j} + 12)}{2s} = 0 \quad (=)$$

$$= 60 + V_1\text{j} - \frac{V_1(15 - 8\text{j})}{2s} = 0 \quad (=)$$

$$= 60 + V_1\text{j} - \frac{V_1(3 - 8\text{j})}{s} = 0 \quad / \cdot s \quad (=)$$

$$= s\text{j}V_1 - V_1(3 - 8\text{j}) = -300 \quad (=) \quad 3 + 4\text{j}$$

$$\Rightarrow V_1(s\text{j} - 3 + 8\text{j}) = -300 \Rightarrow V_1 = \frac{-300}{-3 + 4\text{j}} = \frac{300}{3 - 4\text{j}} =$$

$$= \frac{300(3 + 4\text{j})}{2s} = 12(3 + 4\text{j})$$

$$i_A = \frac{-j12(3 + 4\text{j})}{10} = \frac{6(-3\text{j} + 4)}{s} \quad (=) \quad i_1 = i_g - i_A = 6 - \frac{6(4 - 3\text{j})}{s} = \frac{6 + 18\text{j}}{s}$$

$$P = \frac{1}{2} |i|^2 \cdot R = \frac{1}{2} \cdot 30 \cdot \left(\frac{6(1 + 3\text{j})}{s} \right)^2 = 3 \cdot \frac{36 \cdot (1 + 6\text{j} - 9)}{s} = \frac{108(-8 + 6\text{j})}{s} = \frac{-216(4 - 3\text{j})}{s}$$

3. A 400 Hz sinusoidal voltage with a maximum amplitude of 100 V at $t = 0$ is applied across the terminals of an inductor. The maximum amplitude of the steady-state current in the inductor is 25 A.

- a) What is the frequency of the inductor current? 400 Hz
- b) If the phase angle of the voltage is zero, what is the phase angle of the current? 90°
- c) What is the inductive reactance of the inductor? $4\ \Omega$
- d) What is the inductance of the inductor in millihenry (mH)? $\frac{4}{2\pi \cdot 400} = \frac{1}{2\pi \cdot 100} = \frac{1}{2\pi} \cdot 10^{-2} = \frac{10}{2\pi} \cdot 10^{-3} = \frac{5}{\pi} \text{ mH}$
- e) What is the impedance of the inductor? $4\ \Omega$

$$400\text{ Hz} = 1 \cdot 2\pi = 400\text{ rad/s}$$

